

Department Of Engineering and Physics  
 Bachelor of Science (Honours) in Agricultural Engineering  
 Electrical and Electronic Principles

3 HOURS (100 MARKS)

INSTRUCTIONS

Answer any **FOUR** questions. Each question carries 25 marks.

**Question 1**

- a. Distinguish between conventional current and electrical current. [2 marks]
- b. A circuit consists of four 100 W lamps connected in parallel across a 230 V supply. Inadvertently, a voltmeter has been connected in series with the lamps. Determine the voltmeter reading if the resistance of the voltmeter is  $1500 \Omega$  and that of the lamps under the conditions stated is six times their value when burning normally. [8 marks]
- c. With the aid of diagrams, describe five sources of electricity. [15 marks]

**Question 2**

- a. For the circuit shown in Figure 1, determine
  - i. Charges on the capacitors, [6 marks]
  - ii. Potential difference across the capacitors. [4 marks]

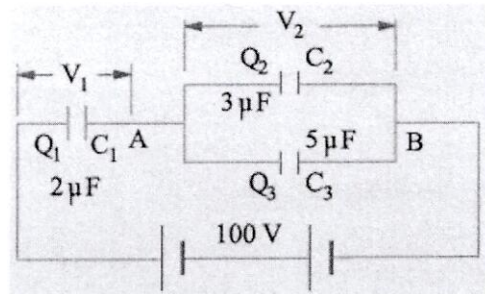


Figure 1

- b. Explain five reasons behind high current losses in alternating current circuits than in direct current circuits. [15 marks]

**Question 3**

- a. Explain the effects of temperature on resistances of pure metals and semi-conductors. [4 marks]
- b. A piece of silver wire has a resistance of  $1 \Omega$ . Calculate the resistance of manganin wire of one-third the length and one-third the diameter, if the specific resistance of manganin is 30 times that of silver. [9 marks]
- c. With the aid of neat sketches, explain the four effects of an electric current. [12 marks]

**Question 4**

- a. Explain the Kirchhoff's laws as used in direct current circuits. [6 marks]  
 b. Determine the current supplied by each battery in the circuit shown in Figure 2. [10 marks]

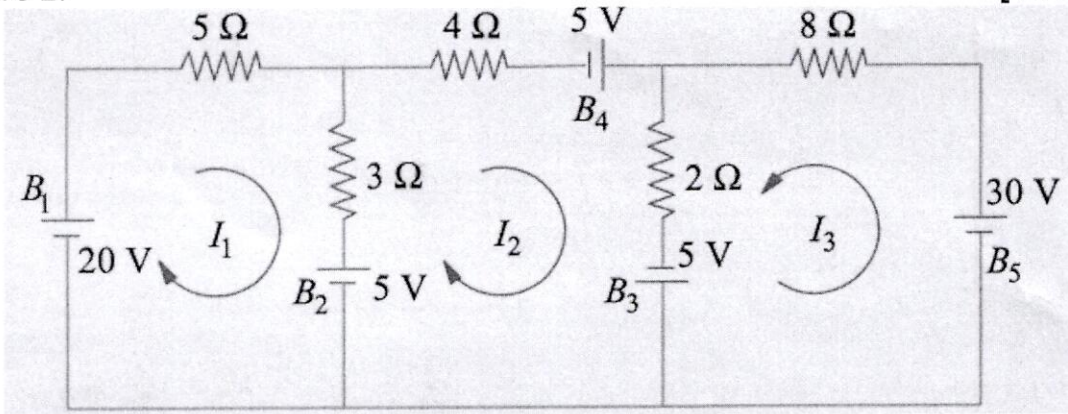


Figure 2

- c. In the circuit of Figure 3, find current through 1-Ω resistor using:  
 i. The Thevenin's theorem and [4 marks]  
 ii. The Superposition theorem. [5 marks]

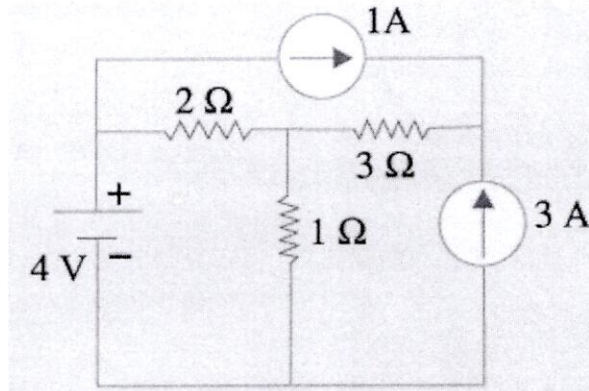


Figure 3

**Question 5**

- a. An hydro-electric station has a turbine of efficiency 86% and a generator of efficiency 92%. The effective head of water is 150 m. Calculate the volume of water used when delivering a load of 40 MW for 6 hours. [8 marks]  
 b. The small identical conducting spheres have charges of  $2.0 \times 10^{-9} \text{ C}$  and  $-0.5 \times 10^{-9} \text{ C}$  respectively. When they are placed 4 cm apart, calculate:  
 i. the force between them, [4 marks]  
 ii. the force between them when they are brought into contact and then separated by 4 cm. [5 marks]  
 c. A 120- $\mu\text{F}$  capacitor is connected across a 415-V, 50-Hz supply. Calculate:  
 i. the reactance offered by the capacitor, [3 marks]  
 ii. the maximum current and [2 marks]  
 iii. the r.m.s. value of the current drawn by the capacitor. [3 marks]

**Question 6**

- a. With the aid of diagrams, describe the two types of bipolar junction transistors. [8 marks]

b. Simplify and prepare a truth table for a Boolean function given as

$$Z = ABC + ABC\bar{C} + A\bar{B}C$$

[5 marks]

c. Write the Boolean expressions and work out the truth tables for the logic circuits in Figure 4 and Figure 5.

[12 marks]

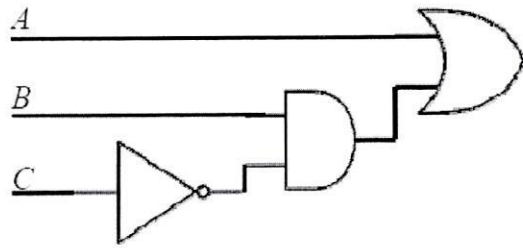


Figure 4

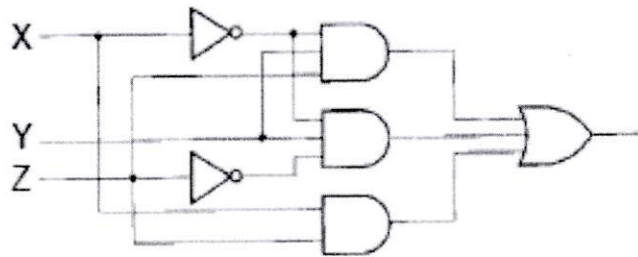


Figure 5

End of paper