

# BINDURA UNIVERSITY OF SCIENCE EDUCATION

## PHYSICS AND ENGINEERING DEPARTMENT

### PH206: ELECTRONICS 1

TIME: 3 HOURS

#### INSTRUCTIONS

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

#### Physical constants

Electronic charge,  $e = 1.6 \times 10^{-19} \text{ C}$

Boltzmann's constant,  $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$

#### SECTION A

- 1 (a) Distinguish between ideal and practical sources in electric circuit theory. [2]
- (b) Use resistor colour codes to determine the resistances of resistors with the following band colours:
- (i) green, brown, blue, silver. [2]
- (ii) yellow, violet, silver. [2]
- (iii) grey, red, gold. [2]
- (c) The Shockley ideal diode equation can be used to express the net current  $I$  flowing through a diode as a function of the voltage  $V$  applied across the diode terminals as:
- $$I = I_0 \left( e^{\frac{qV}{kT}} - 1 \right)$$
- where symbols have their usual meanings.
- (i) Define the symbols used. [3]
- (ii) Calculate the thermal voltage across the diode at 298 K. ( $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$ ). [3]
- (d) List any four major properties of ideal op-amps. [4]
- (e) The instantaneous current of an ac sinusoidal current is given by  $i = I_m \cos \omega t$ . Show that  $I_{rms} = \frac{I_m}{\sqrt{2}}$ . [6]
- (f) A sinusoidal voltage signal is represented by  $v = 30 \sin 150\pi t$ . Calculate frequency of the voltage signal? [6]

- (g) A  $2.0\text{ H}$  inductor and a  $30\ \Omega$  resistor are connected in series with an a.c. voltage source. The voltage across the inductor is given as  $v = 100 \sin 20t$ . Determine the root mean square value of the applied voltage. [6]
- (h) Calculate the frequency at which an inductor of  $50\text{ mH}$  has the same reactance as a capacitor of  $470\ \mu\text{F}$ . [4]

### SECTION B

- 2 For the network shown in Fig. 2.1, find the equivalent resistance  $R_{ab}$  and the current  $i$  using the Wye-Delta transformation. [20]

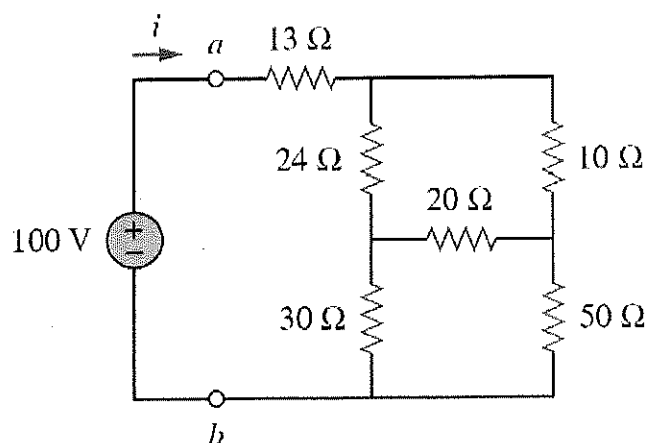


Fig. 2.1

- 3 (a) Determine the current through  $6\ \Omega$  resistor in the circuit in Fig. 3.1 using Norton's theorem. [16]

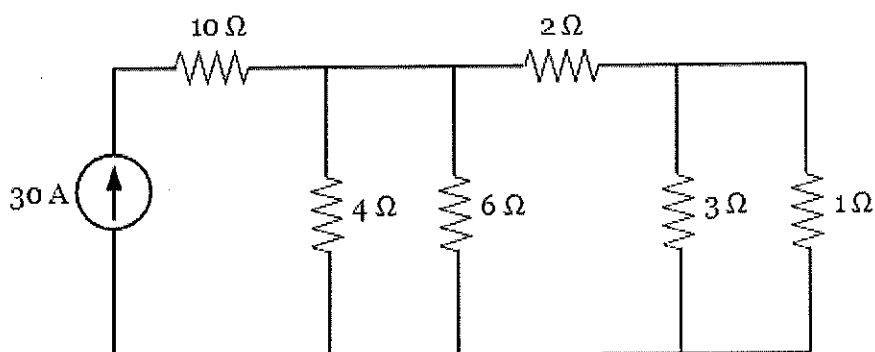


Fig. 3.1

- (b) Calculate the amount of heat energy dissipated in the  $6\ \Omega$  resistor in part (a) over a time interval of 1 hour. [4]

- 4 (a) In the network of Fig. 4.1, find the current through the  $6\ \Omega$  resistor using Thevenin's Theorem. [16]

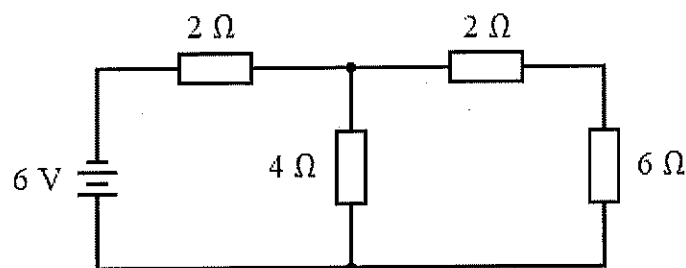


Fig. 4.1

- (b) Calculate the potential difference across and the power dissipated in the  $6\ \Omega$  resistor in part (a). [4]
- 5 (a) Determine the current through the  $4\ \Omega$  resistor in the circuit in Fig. 5.1 using Mesh analysis. [16]

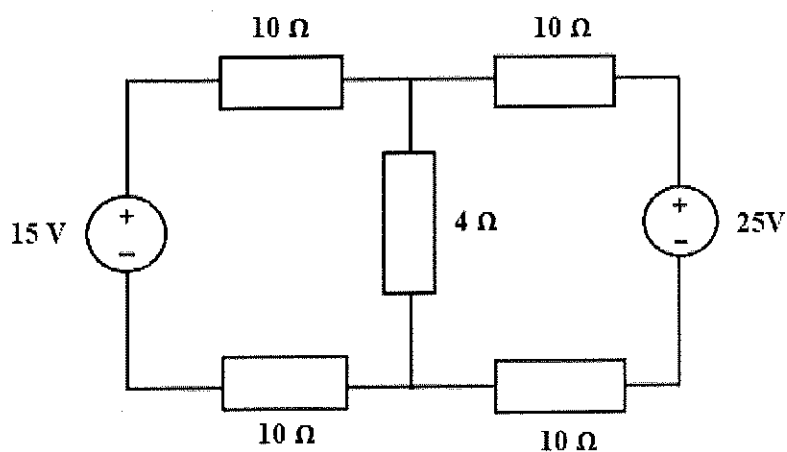


Fig. 5.1

- (b) Hence calculate the voltage across the  $4\ \Omega$  resistor. [4]

- 6 A voltage source is connected to a resistor, capacitor and an inductor as shown in Fig. 6.1.

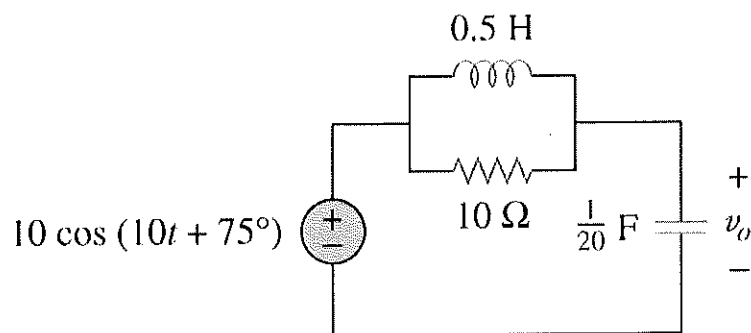


Fig. 6.1

- (a) Express  $10 \cos(10t + 75^\circ)$  in phasor form. [2]
- (b) Determine the voltage  $v_o$  across the capacitor giving your answer in time domain. [18]