

BINDURA UNIVERSITY OF SCIENCE EDUCATION

FACULTY OF SCIENCE AND ENGINEERING

DEPARTMENT OF ENGINEERING AND PHYSICS

Bachelor of Sciences Honours Degree in Electronic Engineering

EEEE1103: ELECTRICAL ENGINEERING CIRCUITS AND ANALYSIS

DURATION: 3 hours

TOTAL MARKS: 100

2 OCT 2024

INSTRUCTIONS

The paper contains SEVEN questions each carrying 20 marks

Answer FIVE questions

QUESTION 1

- a) A flashlight battery has a rating of 0.8 ampere-hours (Ah) and a lifetime of 10 hours.
- i. How much current can it deliver? [2]
 - ii. How much power can it give if its terminal voltage is 6 V? [2]
 - iii. How much energy is stored in the battery in kWh? [2]
- b) A coil has an inductance of 40mH and a negligible resistance. If connected to a 240V, 50Hz supply calculate its
- i. Inductive reactance. [2]
 - ii. Resulting current. [2]
- c) With the aid of a diagram clearly show how a Thevenin equivalent circuit can be converted to a Norton equivalent circuit and vice versa. [4]
- d) Find I and V_o in the circuit of Figure 1.1. [6]

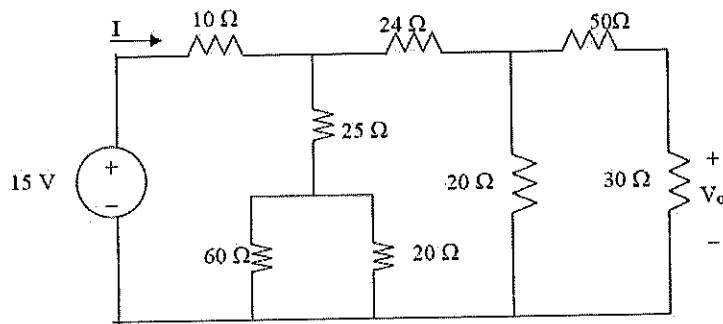


Figure 1.1

QUESTION 2

- a) Use superposition to find v in the circuit of Fig. 2.1

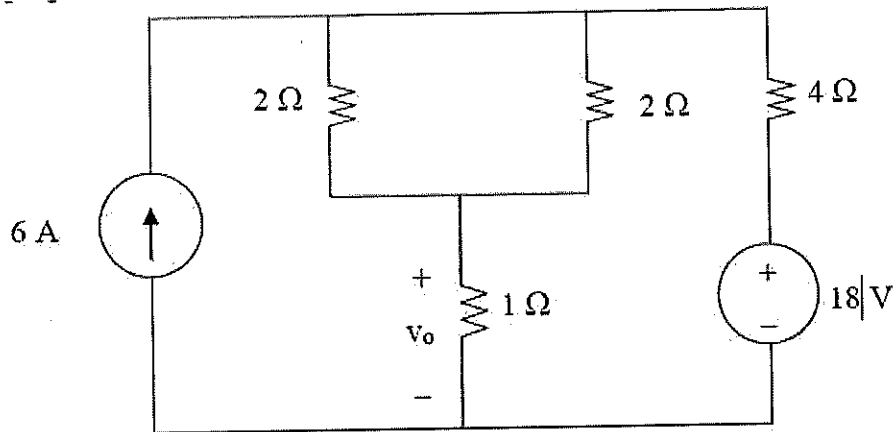


Figure 2.1

[6]

- b) If $V_{ab} = 400$ V in a balanced Y-connected three-phase generator, find the phase voltages, assuming the phase sequence is *abc*. [3]
- c) A d.c motor consumes 47.50 MJ when connected to a 250V supply for 1 hour 45 minutes. Determine the power rating of the motor. [2]
- d)

$$v(t) = 56e^{-200t} \text{ V}, t > 0$$

$$i(t) = 8e^{-200t} \text{ mA}, t > 0$$

- i. Find the values of R and C . [3]

- ii. Calculate the time constant τ . [3]
- iii. Determine the time required for the voltage to decay half its initial value at $t = 0$. [3]

QUESTION 3

- a) Transform the following sinusoids to phasors:
 - i. $-10 \cos(4t + 75^\circ)$. [2]
 - ii. $5 \sin(20t - 10^\circ)$. [2]
 - iii. $4 \cos 2t + 3 \sin 2t$. [2]
- b) A current source in a linear circuit has $I_s = 8 \cos(500\pi t - 25^\circ)$ A
 - i. What is the amplitude of the current? [1]
 - ii. What is the angular frequency? [1]
 - iii. Find the frequency of the current. [1]
 - iv. Calculate I_s at $t = 2$ ms. [2]
- c) Series-connected 20-pF and 60-pF capacitors are placed in parallel with series-connected 30-pF and 70-pF capacitors. Determine the equivalent capacitance. [3]
- d) Use the mesh analysis to determine the current through the 9V battery show in the Fig 3.1 below. [6]

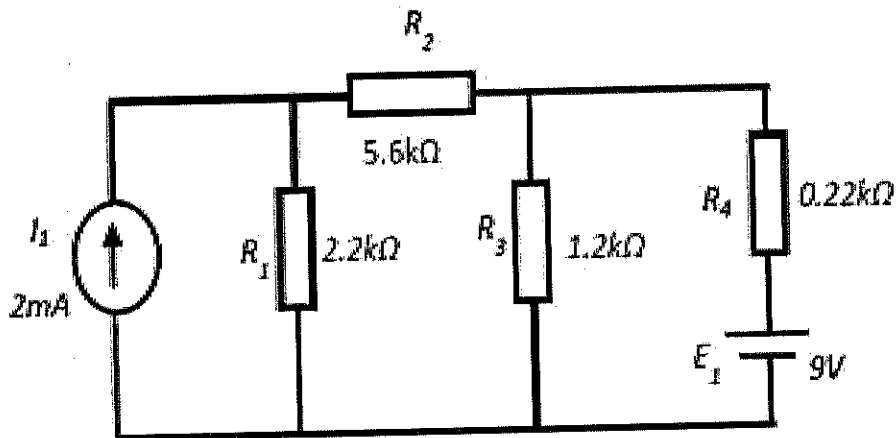


Figure 3.1

QUESTION 4

- a) Consider the circuit shown below in Fig 4.1 and calculate V_o . [5]

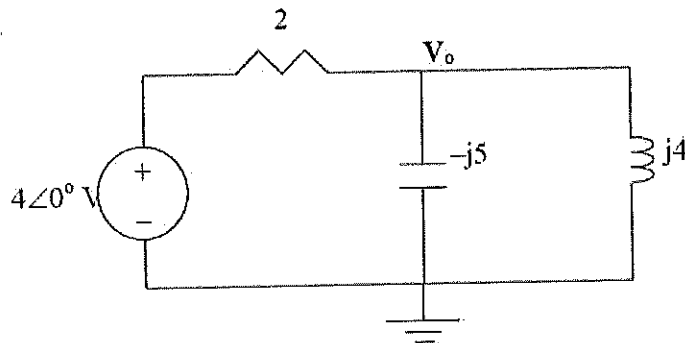


Figure 4:1

- b) An energy-storage network consists of series-connected 16-mH and 14-mH inductors in parallel with a series connected 24-mH and 36-mH inductors. Calculate the equivalent inductance. [5]
- c) With the help of diagrams, show the difference between an open circuit and short circuit. [5]
- d) Calculate the root mean square value for the voltage given by $v_e = 550\sin(377t - 50)$. [3]
- e) What is stray capacitance. [2]

QUESTION 5

- a) Give statements of the following laws.
- Faraday's law of electromagnetic induction [2]
 - Lenz's law. [2]
- b) Draw a sketch of power against time with supporting equations of the following:
- Inductive load. [3]
 - Resistive load. [3]
 - Capacitive load. [3]
- c) Define the following
- average power. [1]
 - reactive power. [2]

- iii. apparent power. [2]
- iv. power factor. [2]

QUESTION 6

- a) Find the overall power dissipated in the circuit below in Fig 5.1. [5]

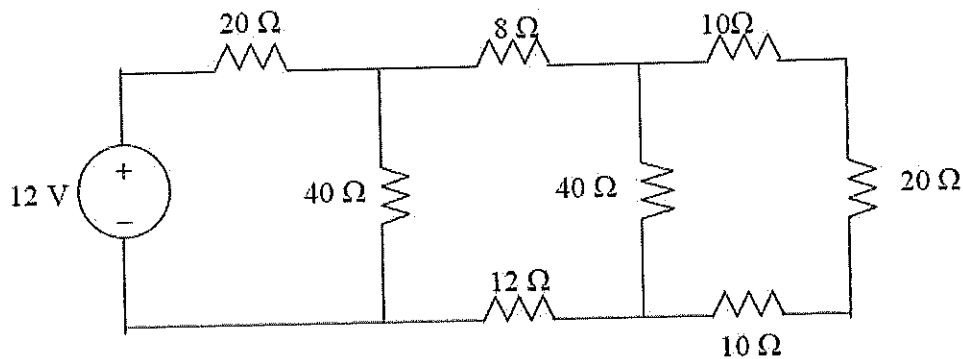


Figure 5:1

- b) An aluminum wire 7,5m long is connected in parallel with a copper wire 6m long. When a current of 5A is passed through the combination, it is found that the current in the aluminum wire is 3A. The diameter of the aluminum wire is 1.0mm. Determine the diameter of the copper wire (Resistivity of copper is $0,017\mu\Omega m$, that of aluminum is $0,028\mu\Omega m$). [6]
- c) Draw the V-I relationship of an ideal voltage source. [5]
- d) Briefly describe what is hysteresis. [4]

QUESTION 7

- a) Find the Norton equivalent as viewed from the terminals of the circuit in Fig.6.1. [10]
- i. a-b.
 - ii. c-d.

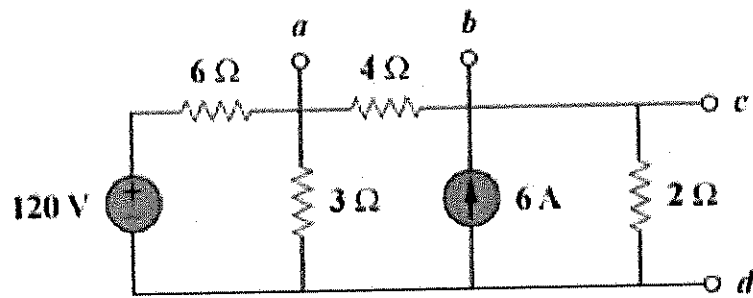


Figure 6:1

- b) Find the frequency domain impedance Z as shown in the Fig 7.1 below. [7]

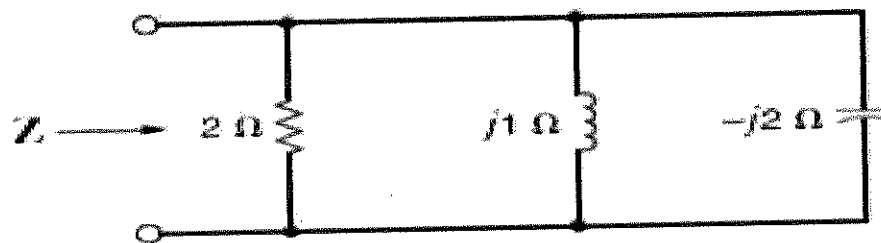


Figure 7:1

- c) What is rms value. [3]

THE END