

BINDURA UNIVERSITY OF SCIENCE EDUCATION

FACULTY OF SCIENCE EDUCATION

DEPARTMENT OF ENGINEERING AND PHYSICS

PROGRAMME: Bachelor of Science Honours Degree in Electronic Engineering

EEE5202/EEE4202(2): RF and MICROWAVE DEVICES and Circuits

Duration: 3 Hours Total Marks: 100

INSTRUCTIONS TO CANDIDATES

1. Answer any five (5) questions
2. The paper contains **SEVEN (7)** questions
3. Marks are shown in brackets

5 JUN 2025

INSTRUCTIONS TO CANDIDATES

1. Answer any five (5) questions
2. The paper contains **SEVEN (7)** questions
3. Each question carries twenty (20) marks
3. Marks are shown in brackets

Constants: $\mu_0 = 4\pi \times 10^{-7} \text{ F/m}$, $\epsilon_0 = 8.854 \times 10^{-12} \text{ H/m}$

Question 1


- (a) Using examples, state four applications of microwaves. [4]
- (b) Justify why microwaves are suitable for the applications above. [4]
- (c) State any two disadvantages of microwaves. [2]
- (d) In what way are Microwaves different from Low-Frequency Signals? [4]
- (e) Giving examples of each, state three key components that are found in a microwave system. [6]

Question 2

- (a) State two functions of IEEE commonly used microwave frequency bands. [3]
- (b) With the aid of S-parameters or S-matrices, state any three properties of S-parameters. [6]
- (c) Outline the significance of S-parameters in analysing microwave networks. [3]
- (d) Draw the high-frequency equivalent circuit of an inductor. Account for C and R. [3]
- (e) State two typical applications of a directional coupler. [2]
- (f) A lossy cable with $R = 2.5 \Omega/\text{m}$, $L = 10 \text{ mH/m}$, $C = 10 \text{ pF/m}$ and $G = 0$ operates at $f = 1\text{GHz}$. Find the attenuation constant of the line. [3]

Question 3

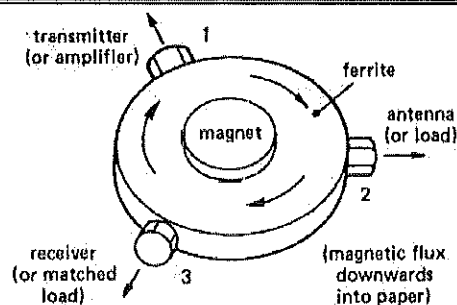- (a) (i) Name the microwave passive component below and describe how it operates. [5]



(b) A plane wave of frequency 1 GHz frequency is travelling in a block of Teflon where $\epsilon_r = 2.1$, $\mu_r = 1$ and $\sigma = 0$. Determine:

- (i) Phase constant. [1]
- (ii) Intrinsic impedance. [1]
- (iii) Wavelength. [1]
- (iv) Phase velocity. [1]

(c) A two-port network is known to have the following scattering matrix:

$$[S] = \begin{bmatrix} 0.15 \angle 0^\circ & 0.85 \angle -45^\circ \\ 0.85 \angle 45^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$

- (i) Determine if the network is reciprocal and lossless. For each case give a reason by calculation or otherwise. [3]
- (i) If a port 2 is terminated with a matched load, what is the return loss seen at port 1? [3]
- (d) Deduce the range of SWR and Γ of a transmission line? [4]

Question 4

- (a) Briefly describe how a Microwave Oven Work? [2]
- (b) Which component is represented by the scattering matrix $\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$? [2]
- (c) Differentiate an isolator from a circulator [2]
- (d) Write down the S-matrix of a three-port circulator. [3]
- (e) In a two-way communication, the transmitter transmits an output power of 100W at 10 GHz. The transmitting antenna has a gain of 36 dB, and the receiving antenna has a gain of 30 dB. What is the received power level at a distance of 40 km (a) if there is no system loss and (b) if the system loss is 10 dB? [7]
- (f) The incident power is 100 W for a directional coupler. It has a coupling factor of 25 dB and a directivity of 40 dB. Find coupled and isolated port powers. [4]

Question 5

- (a) If H field is given by $H(z,t) = 48 \cos(10^8 t + 40z) \mathbf{a}_y$ A/m. Calculate or identify the following:
 - i. Amplitude. [1]
 - ii. Frequency. [1]
 - iii. Phase constant. [1]
 - iv. Wavelength. [1]
- (b) Calculate the voltage reflection coefficient at the terminating end of a transmission line with a characteristic impedance of 50 Ω when it is terminated by:
 - (i) A 50 Ω termination. [1]
 - (ii) An open-circuit termination. [1]
 - (iii) A short circuit termination. [2]

- (c) A 300 m long line has the following constants: $R = 4.5 \text{ k}\Omega$, $L = 0.15 \text{ mH}$, $G = 60 \text{ Siemens}$, $C = 12 \text{ nF}$, operated at a frequency 6 MHz. Find the propagation constant, characteristic impedance and velocity of propagation. [6]
- (d) Of the passive microwave devices you studied, state any two two-port devices? [2]
- (e) State boundary conditions at the interface between free space and an antenna. [4]

Question 6

- (a) What are the basic parameters used to measure the performance of a directional coupler? [4]
- (b) A lossless 75 W transmission line is terminated by an impedance of $150 + j150 \Omega$. Using the Smith chart, find (a) VSWR, and (b) reflection coefficient. [5]
- (c) Name some wave guide components used to change the direction of the guide through an arbitrary angle [3]
- (d) Determine the S parameters for a reciprocal and lossless network, perfectly matched 2-port network. [4]
- (e) Draw a well labelled diagram of a four-port directional coupler showing power flow [4]

Question 7

The S-parameters can be measured using commercial test sets such as the network analyzer.

- (a) Draw a diagram that can be used to measure S_{11} and S_{22} . [6]
- (b) What is Tee junction with reference to passive microwave components? Give two examples [3]
- (c) The block diagram of a wireless receiver front-end is shown in Figure1 below. Compute the overall noise figure of this subsystem. If the input noise power from a feeding antenna is $N_i = kT_A B$, where $T_A = 150 \text{ K}$, find the output noise power in dBm. If we require a minimum signal-to-noise ratio (SNR) of 20 dB at the output of the receiver, what is the minimum signal voltage that should be applied. [8]

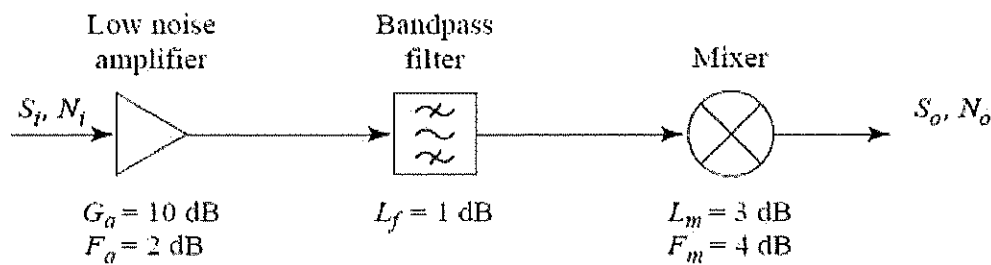


Figure 1 Block diagram of a wireless receiver front-end

- (d) Using examples of typical applications state what is meant by the term microwave engineering. [3]

END OF EXAMINATION

The Complete Smith Chart

Black Magic Design

