

**BINDURA UNIVERSITY OF SCIENCE EDUCATION**

**PHYSICS AND ENGINEERING DEPARTMENT**

**PH115: DIGITAL LOGIC**

**TIME: 3 HOURS**

JUN 2023

**INSTRUCTIONS**

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

**SECTION A**

1. a. Concisely describe the major differences between analogue and digital quantities. [4]
- b. i. What is the next binary number following  $10111_2$  in the counting sequence? [2]  
ii. What is the largest decimal value that can be represented using 12 bits? [2]
- c. Convert the following binary coded decimal (BCD) number to its decimal Equivalent: 0110100000111001. Comment on your finding. [5]
- d. i. What is a truth table? [2]  
ii. What is the only set of input condition that will produce a LOW output for any OR gate? [2]
- e. i. What is the advantage of a synchronous counter over an asynchronous Counter? What is the disadvantage? [4]  
ii. How many logic devices are required for a MOD-64 parallel counter? State them. [4]  
iii. What Logic signal drives the J, K. inputs of the MSB flip-flop for the counter in 1(e)(ii)? [2]
- f. Define the following terms:  
i. Magnitude comparator [3]  
ii. Multiplexers [3]  
iii. Demultiplexers [3]
- g. iv. Distinguish between a *serial in/parallel out* register and a *serial in/serial out* register. [4]

**SECTION B**

2. a. State whether each of the following is a digital or analogue quantity:  
i. Number of atoms in a sample of material [1]  
ii. Altitude of an aircraft [1]  
iii. Pressure in a bicycle tyre [1]  
iv. Current through a speaker [1]  
v. Time setting on a microwave [1]
- b. Draw a timing diagram for a digital signal that continuously alternates between 2.0V (binary 0) for 2milli-seconds (ms) and 4.4V for 4ms. [5]

- c. Convert each of the following octal numbers to its decimal equivalent:
- 36
  - 1655 [1]
  - 1204 [1]
  - 5 [1]
- d. Convert each of the following decimal numbers to octal:
- 372 [1]
  - 771 [1]
  - 255 [1]
- e. Convert each of the following octal values to binary:
- 36 [1]
  - 1655 [1]
  - 1204 [1]
3. a. Write the expression for the output of figure 1, and use it to determine the complete truth table. [6]

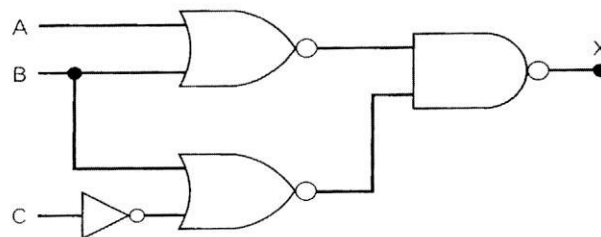


Figure 1: Combinational circuit

- b. i. Show how a two-input NAND gate can be constructed from two-input NOR gates. [4]
- ii. Show how a two-input NOR gate can be constructed from two-input NAND gates. [4]
- c. Under what conditions will:
- an OR gate allows a logic signal to pass through to its output unchanged? [2]
  - an AND gate allows a logic signal to pass through to its output unchanged? [2]
  - a NOR gate allows a logic signal to pass through to its output unchanged? [2]
4. a. i. Draw a NAND Latch and its truth table. For a NAND Latch what is the Normal state of the  $\overline{SET}$  and  $\overline{CLEAR}$  inputs? [8]
- b. Add the following in binary. Check your results by doing the addition in decimal.
- $1010 + 1011$  [2]
  - $1111 + 0011$  [2]
  - $1011.1101 + 11.1$  [2]
  - $0.1011 + 0.1111$  [2]
- c. Find the sum of each of the following pairs of hex numbers:
- $3E91 + 2F93$  [2]
  - $91B + 6F2$  [2]

5. a. In figure 2 below change each AND gate to an OR gate, and change the OR gate to an AND gate. Then write its expression for output x [4]

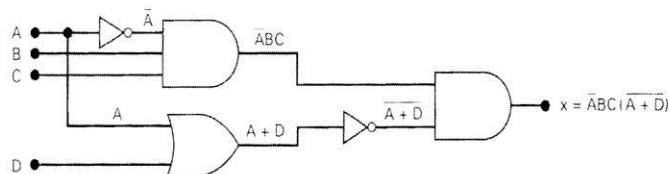


Figure 2: Combinational Logic expression

- b. Draw the circuit diagram to implement the expression:  $x = (A+B)(\bar{B}+C)$ . Explain how you figure out. [4]
- c. i. State the two general forms for logic expressions. [2]  
 ii. Outline the approach or steps you would take to design a combinational logic circuit. [4]
- d. Clearly distinguish between an exclusive-OR and an exclusive-NOR circuit by their respective expressions and stating when each of them has HIGH output. [6]
6. a. What is meant by the following: [3]  
 i. D Latch circuit [3]  
 ii. A one-shot. [3]
- b. Outline principal uses of FFs [5]
- c. What are the effects of a Schmitt-trigger type of input to a circuit? [5]
- d. Give the meaning of the following digital system terms: [2]  
 i. Data bus [2]  
 ii. Tristate outputs [2]

**END OF EXAMINATION**