

BINDURA UNIVERSITY OF SCIENCE EDUCATION

FACULTY OF SCIENCE AND ENGINEERING

DEPARTMENT OF ENGINEERING AND PHYSICS

JUN 2024

Bachelor of Science Honours Degree in Electronic Engineering

**EEN 5102:**

**Integrated Circuits and Microelectronics**

**Duration: 3 hours**

**Total marks: 100**

### INSTRUCTIONS

This paper contains seven questions each carrying 20 marks.


Answer any **FIVE** questions.

### Question 1


- a) (i) State the three different classes of integrated circuits according to structure. [3]
- (ii) Hence list the advantages and disadvantages of each. [9]
- b) Highlight the different classes of Integrated circuits according to function. [2]
- c) With reference to Integrated circuits, distinguish between passive and active components giving a typical example of each. [4]
- d) Distinguish between an Integrated circuit and a discrete circuit. [2]

### Question 2

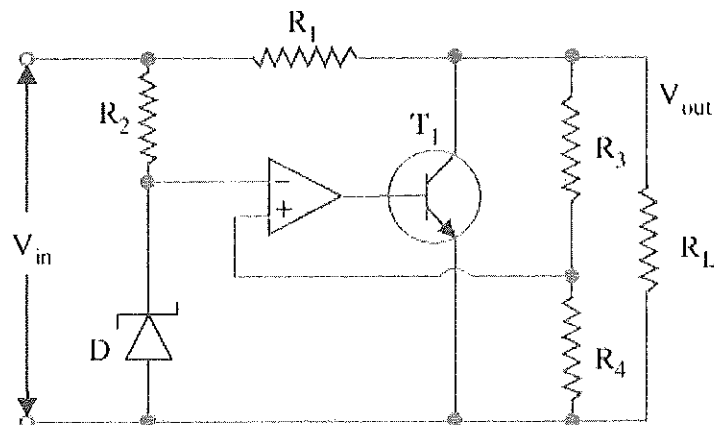- a) Describe how voltage regulation is achieved in the circuit below. [5]



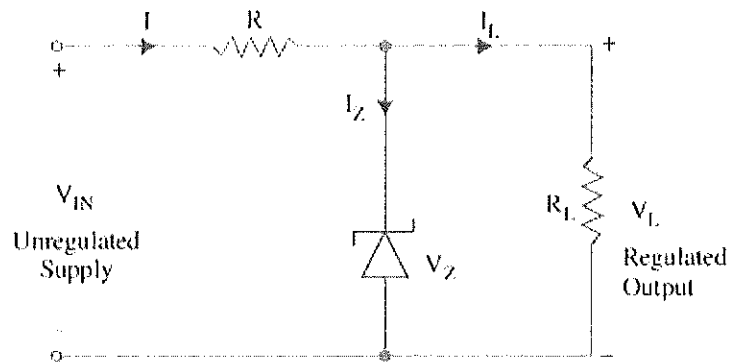- b) The Zener diode in figure below has the following ratings,  $V_z = 6.8\text{V}$  at  $I_z = 50\text{ mA}$ ,  $r_z = 2\ \Omega$  at  $I_z = 50\text{ mA}$ ,  $I_{z(\text{min})} = 5\text{ mA}$ ,  $I_{z(\text{max})} = 150\text{ mA}$ . What would be the load voltage when the load current  $I_L$  varies from 10 mA to 120 mA. Also, calculate voltage regulation of the regulator. [5]




c) With the aid of a circuit diagram, describe the operation of the step-up switching voltage regulator. [10]

### Question 3

a) Describe the following terms/sections as used by the computer in the monitoring and controlling of a physical variable (that is assumed to be analog) in process control. Give examples where possible.

- (i) Transducer. [3]
- (ii) Analog-to-digital converter (ADC). [3]
- (iii) Computer. [3]
- (iv) Digital-to-analog converter (DAC). [2]
- (v) Actuator. [2]

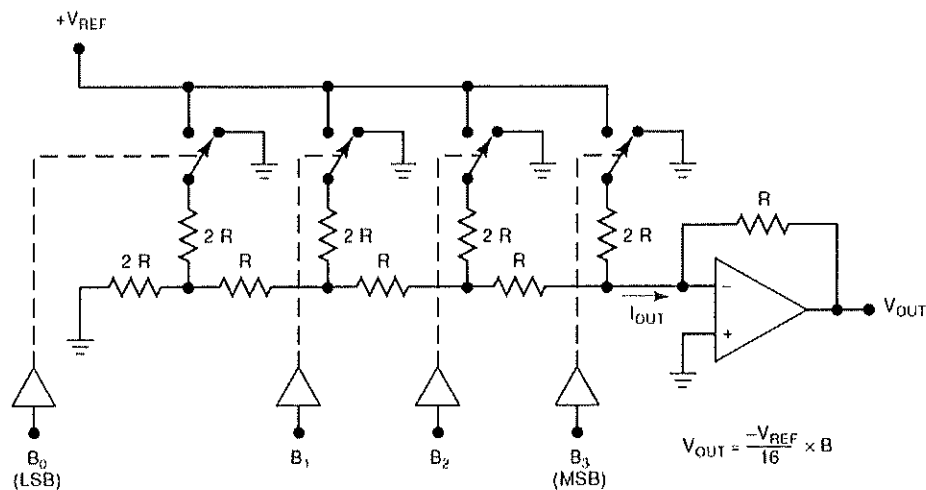
b) Consider the circuit below, and assume that  $V_{REF} = 10$  V for the Digital to Analogue converter (DAC). What are the resolution and full-scale output of this converter? [4]




- c) A five-bit DAC has a current output. For a digital input of 10100, an output current of 10 mA is produced. What will  $I_{OUT}$  be for a digital input of 11101? [3]

#### Question 4

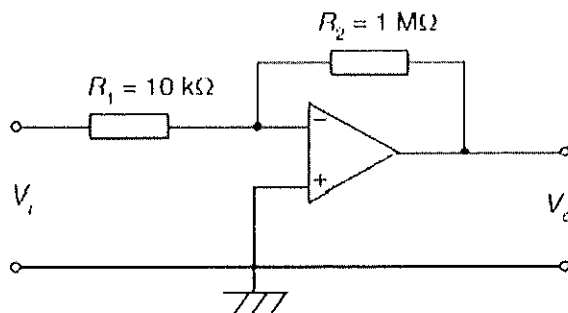- a) Highlight the three main properties of an op amp. [3]
- b) Determine the common-mode gain of an op amp that has a differential voltage gain of  $150 \times 10^3$  and a CMRR of 90 dB. [3]
- c) The op amp shown in Figure below has an input bias current of 100 nA at 20°C. Calculate:
- the voltage gain. [1]
  - the output offset voltage due to the input bias current. [2]
  - How can the effect of input bias current be minimized? [2]



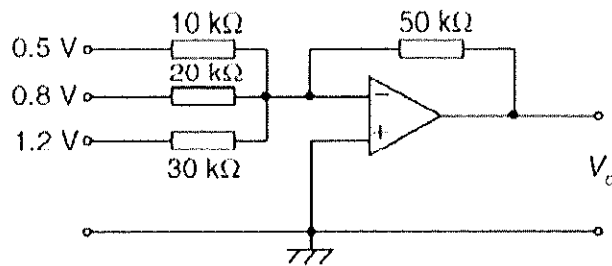- d) For the summing op amp shown in figure below, determine the output voltage,  $V_o$ . [3]




- e) With the aid of a circuit diagram and waveforms, explain the principle of operation of the photodiode. [6]

### Question 5

- a) Define Resolution (Step Size) of a D/A converter with the aid of formula. [3]
- b) (i) What is a Phase Locked Loop? [1]
- (ii) With the aid of a block diagram, and typical output signals for every section, briefly explain the operation of the different sections of the Phase Locked Loop. [12]
- c) State any four typical applications of the photodiode. [4]

### Question 6

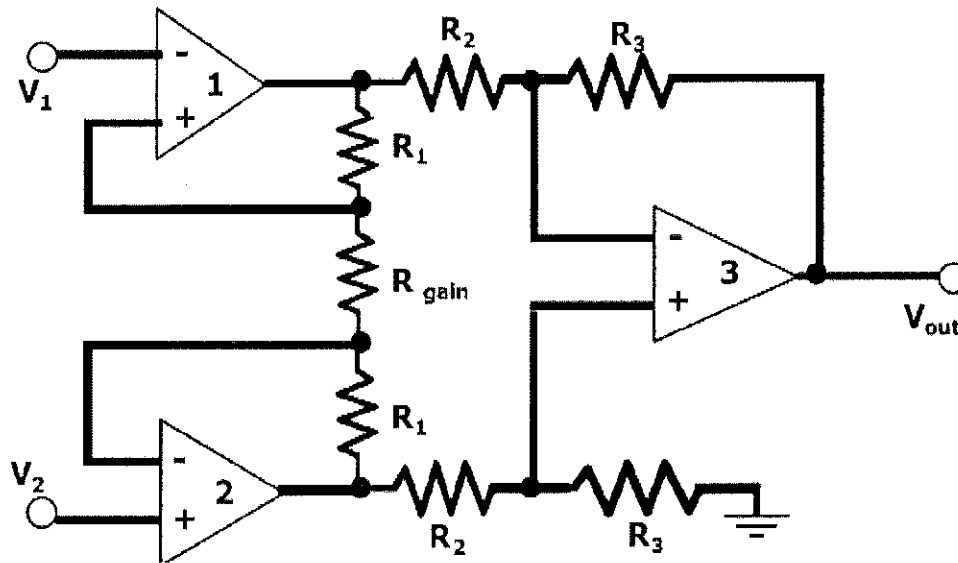- a) With the aid of a circuit diagram of your choice and input/output waveforms, describe how a zero-crossing detector works. [10]
- b) With the aid of supporting equations, derive the relationship between,  $V_{out}$ ,  $V_1$ , and  $V_2$  in the circuit diagram below. [6]



- c) Describe two unique characteristics of the LASER light. [4]

### Question 7

- a) Draw the block diagram representing the different stages for an electrical signal measuring system. Give two examples, where applicable of the parameters or equipment involved per stage. [8]
- b) A resistance strain gage with a gage factor of 2 is fastened to a steel member subjected to a stress of  $1,050 \text{ kg/cm}^2$ . Calculate the change in resistance,  $\Delta R$ , of strain-gate element due to the applied stress. [3]
- c) Describe the principle of operation of the capacitive transducer. [6]
- d) List 3 advantages of optical fibre systems over metallic transmission system. [3]