

**BINDURA UNIVERSITY OF SCIENCE EDUCATION**  
**FACULTY OF SCIENCE AND ENGINEERING**  
**DEPARTMENT: ENGINEERING AND PHYSICS**  
**PROGRAMME BSc HONOURS DEGREE IN COMPUTER SCIENCE**  
**COURSE CODE PH206 (3): ELECTRONICS 1**  
**DURATION: 3 HOURS    TOTAL MARKS: 100**

**INSTRUCTIONS TO CANDIDATES**

Answer question one in Section A and any three questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks

**SECTION A**

- 1 (a) Convert the following from rectangular to polar form:  $C = -6 + j 3$ . [4]
- (b) Determine the sum of  $C_1 = 3 + j 6$  and  $C_2 = -6 + j 3$ . [4]
- (c) Find the product of  $C_1$  and  $C_2$  if  $C_1 = -2 - j 3$  and  $C_2 = 4 - j 6$ . [4]
- (d) Given that  $C_1 = 2 \angle -40^\circ$  and  $C_2 = 7 \angle 120^\circ$ , calculate the product of  $C_1$  and  $C_2$ . [4]
- (e) Transform the following sinusoid in time domain to phasor domain:  $v = -4\sin(30t + 50^\circ)$  V. [5]
- (f) Convert the sinusoid corresponding to the following phasor to time domain:  $I = 12 + j 5$  A. [5]
- (g) The instantaneous current of an ac sinusoidal current is given by  $i = I_m \cos \omega t$ . Show that  $I_{rms} = \frac{I_m}{\sqrt{2}}$ . [6]
- (h) Distinguish between ideal and practical sources in electric circuit theory. [2]
- (i) Use resistor colour codes to determine the resistances of resistors with the following band colours:
  - (1) green, brown, blue, silver. [2]
  - (2) yellow, violet, silver. [2]
  - (3) grey, red, gold. [2]

## SECTION B

- 2 (a) Using the Wye-Delta transformation, determine the resistance between P and Q of the network shown in Fig. 2.1. [20]

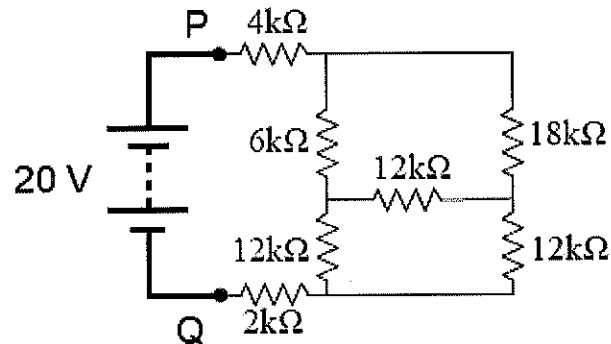


Fig. 2.1

- (b) Calculate the source current. [2]

- 3 (a) Determine the current through the  $1\ \Omega$  resistor in the circuit in Fig. 3.1 using the Superposition Theorem. [17]

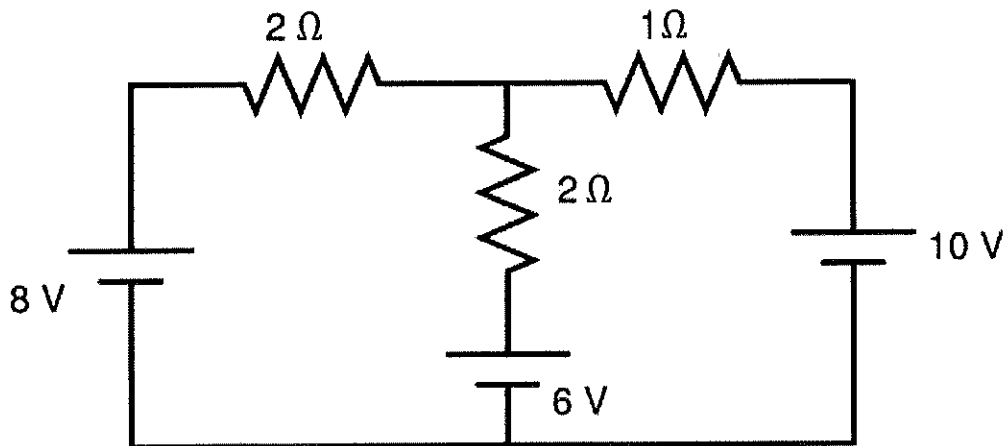


Fig. 3.1

- (b) Calculate the amount of heat energy dissipated in the  $1\ \Omega$  resistor in part (a) over a time interval of 1 hour. [3]

4

In the network of Fig. 4.1, find the Thevenin voltage ( $V_{TH}$ ), Thevenin resistance ( $R_{TH}$ ) and the load current  $I_L$  flowing through and load voltage ( $V_L$ ) across the load resistor  $R_L = 10\ \Omega$  using Thevenin's Theorem. [20]

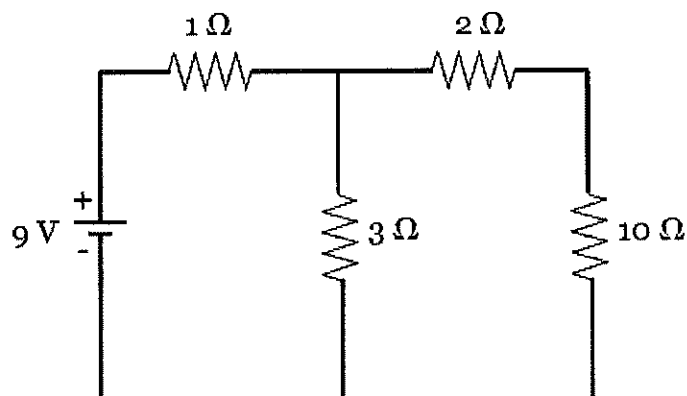


Fig. 4.1

5

In the network of Fig. 5.1, find the Norton current ( $I_N$ ), Norton resistance ( $R_N$ ) and the load current  $I_L$  flowing through and load voltage ( $V_L$ ) across the load resistor  $R_L = 1.5\ \Omega$  using Norton's Theorem. [20]

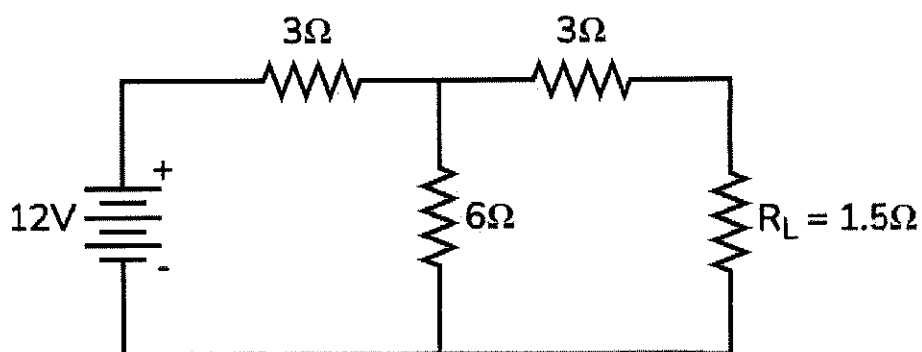


Fig. 5.1

- 6 (a) A  $500\ \mu\text{H}$  inductor,  $80\ \text{pF}$  capacitor and a  $628\ \Omega$  resistor are connected to form a series RLC circuit. Calculate
- (i) the resonant frequency. [4]
  - (ii) Q-factor of this circuit at resonance. [4]
- (b) Find the instantaneous value of alternating voltage  $v = 10 \sin (3\pi \times 10^4 t)$  V at
- (i)  $0\ \text{s}$ . [2]
  - (ii)  $50\ \mu\text{s}$ . [2]
  - (iii)  $75\ \mu\text{s}$ . [2]
- (c) The current in an inductive circuit is given by  $0.3 \sin (200t - 40^\circ)$  A. Obtain the equation for the voltage across it if the inductance is  $40\ \text{mH}$ . [6]