

BINDURA UNIVERSITY OF SCIENCE EDUCATION
PHYSICS AND ENGINEERING DEPARTMENT
PH005: BASIC ELECTRONICS
TIME: 3 HOURS

JUN 2025

INSTRUCTIONS

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

SECTION A

- 1
- (a) Define the term transducer and give any two examples? [3]
 - (b) Discuss the use of light dependent resistors, negative temperature coefficient thermistors and metal wire strain gauges in voltage divider circuits to provide analogue signals. [6]
 - (c) List the four major properties of an ideal op-amp. [4]
 - (d) Negative feedback reduces the gain of the op-amp. Give two reasons why negative feedback is favourable. [2]
 - (e) An inverting operational amplifier has a voltage gain of 50 and it is powered by 6 V. A voltage of 200 mA is applied at its inputs. Calculate the output voltage. [3]
 - (f) Construct a truth table for the EX-NOR gate. [4]
 - (g) Using NAND gates only, show how you can implement the following logic gates:
 - (1) NOT gate. [3]
 - (2) NOR gate. [3]
 - (h) Prove the following Boolean identities using truth tables:
$$(A + B) \cdot (A + C) = A + B \cdot C$$
 [5]
 - (i) Explain why the NAND and NOR gates are said to be universal gates. [2]
 - (j) Construct a logic circuit for the expression $Q = A \cdot (B + C)$ using NAND gates only. [5]

SECTION B

2 Figure 2.1 shows a light sensor circuit and an LDR's data sheet.

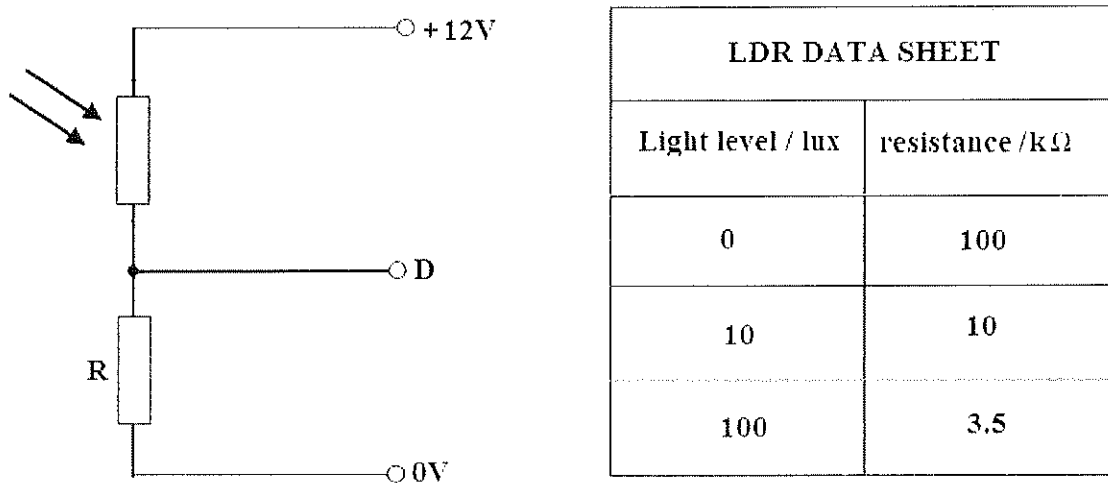


Figure 2.1: Light sensor circuit and the LDR data sheet.

- (a) Suppose you find that the lowest resistance of the LDR in bright sunlight is 100Ω . The LDR maximum power dissipation is 100 mW. Calculate:
 - (i) the maximum current that can flow safely through the LDR in bright sunlight. [3]
 - (ii) the total resistance of the LDR and fixed resistor R, that would limit the current through the LDR to the value found in part (i). [3]
 - (iii) the minimum resistance that could safely be used for R, and then choose the lowest appropriate value from the E24 series. [3]
- (b) Determine the output voltage of the circuit at point X when the light level is:
 - (i) 10 lux. [3]
 - (ii) 0 lux. [3]
- (c) State why the value of resistance chosen in part (a) (iii) is a poor choice for measuring low light levels. [2]
- (d) How would you change the value of R calculated in part (a) (iii) to improve the situation at low light levels? [1]
- (e) The circuit is powered from a 12 V battery of low capacity. State one other advantage of changing the value of R. [2]

3

Figure 3.1 shows part of a comparator circuit.

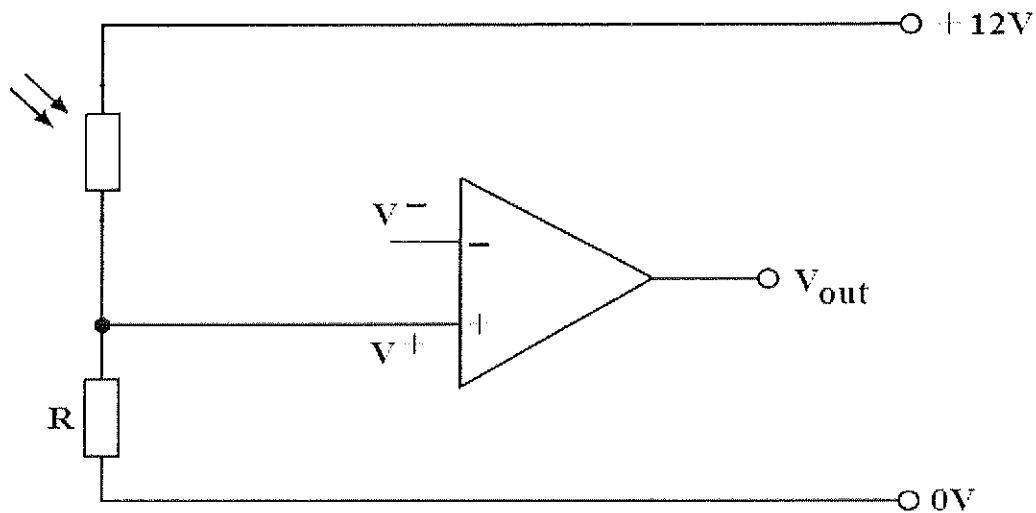


Figure 3.1: Part of a comparator circuit.

- (a) The inverting input V^- requires a reference voltage of 4V.
 - (i) In Figure 3.1 draw two components and their connections to show how this is achieved. [2]
 - (ii) Select suitable values for these components and mark these in Figure 3.1 next to each component. [6]
- (b) The LDR has a maximum power dissipation of 120mW.
 - (i) Calculate the maximum current that could safely flow through the LDR if it had 12V across it. [3]
 - (ii) Calculate the combined resistance of the LDR and R that would allow this current to flow. [3]
 - (iii) The LDR has a minimum resistance of 100Ω in very bright light. Calculate the value of R required if the current calculated in part (b)(i) is not to be exceeded. [2]
- (c) Given that the op-amp used in Figure 3.1 is ideal, state its output voltage when:
 - (i) $V^- > V^+$. [2]
 - (ii) $V^- < V^+$. [2]

4

- (a) A student designs a flood warning system. When the humidity goes above a set level, a signal that operates a siren is produced.
 Draw a system diagram by choosing appropriate input, process, and output subsystems from the list below.
 Alarm (audible warning device), comparator, humidity sensor. [6]
- (b) A student designs a noise warning system to alert the user to the presence of a noise level likely to damage hearing. An LED flashes on and off when the noise level exceeds a safe

value.

- (i) Draw and label each subsystem in Figure 4.1 to show a possible design for the noise warning system using the following subsystems: comparator, LED and sound sensor. [6]

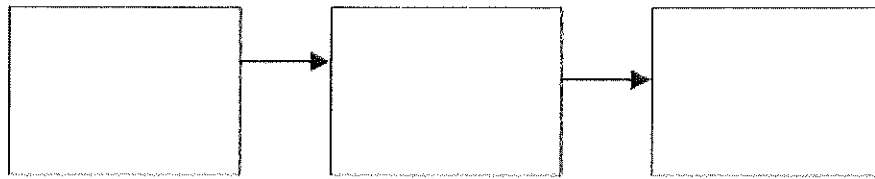


Figure 4.1: A possible design for a noise warning system.

- (ii) In which subsystem could an op-amp be used? [1]
- (c) The comparator circuit diagram is shown in Figure 4.2.

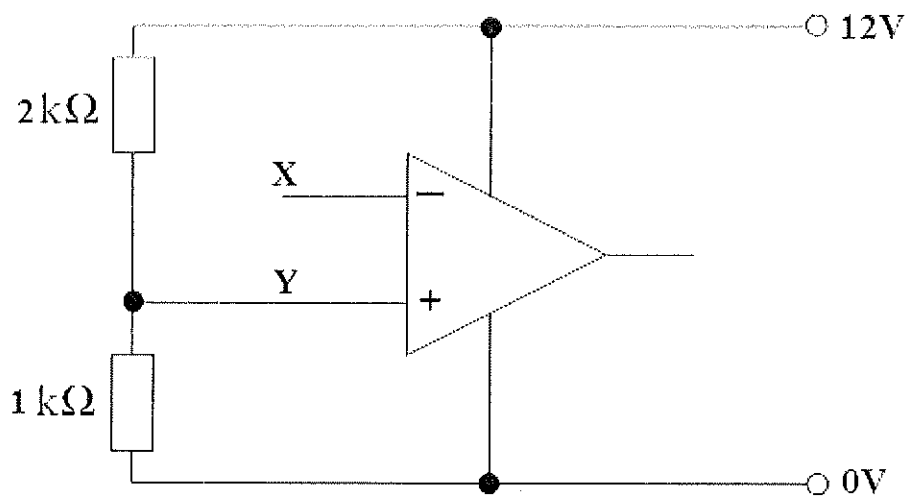


Figure 4.2: The comparator circuit.

- (i) Calculate the voltage at point Y in this circuit. [3]
- The signal from the sound sensor is connected to point X in the comparator circuit. What voltage would you expect from the output of this circuit when
- (ii) the voltage at X is 2V? [2]
- (iii) the voltage at X rises to 6V? [2]

5

(a) Figure 5.1 shows a logic circuit.

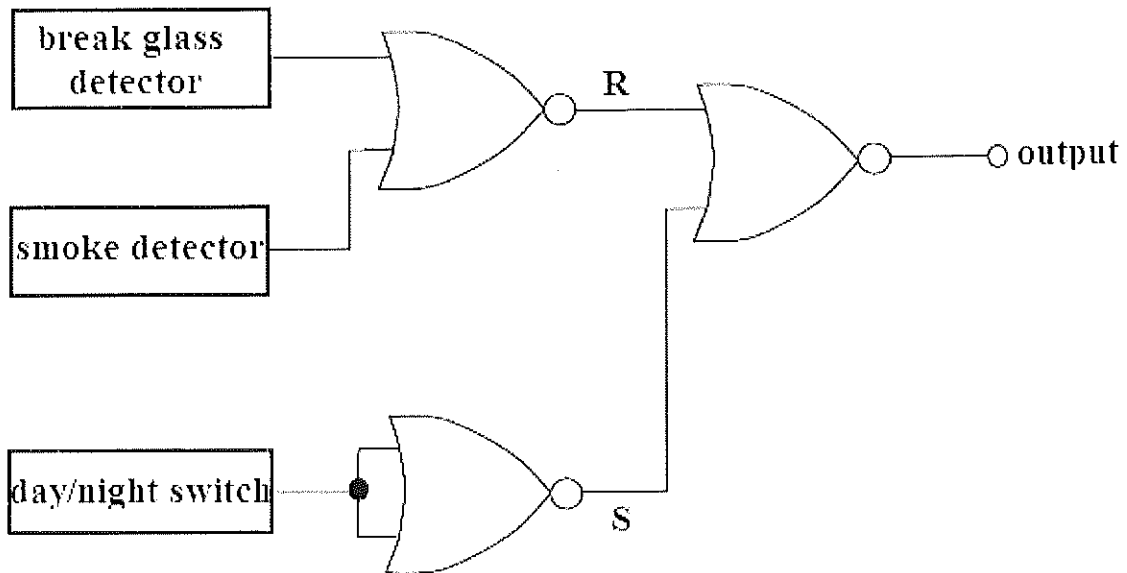


Figure 5.1: Logic circuit.

Copy and complete its truth table shown in Table 5.1.

[18]

Table 5.1: Truth table.

Day/night switch	Break glass detector	Smoke detector	R	S	Output to outside siren
0	0	0			
1	0	0			
0	1	0			
1	1	0			
0	0	1			
1	0	1			
0	1	1			
1	1	1			

(b) Explain whether this proposed system would provide the building with an adequate level of protection.

[2]

- 6 A logic circuit with two inputs X and Y and output Q has the following the Boolean equation:

$$Q = (\overline{X} + \overline{Y}) \bullet (X + Y)$$

- (a) Copy and complete Table 6.1.

[10]

Table 6.1: Truth table.

X	Y	\overline{X}	\overline{Y}	$\overline{X} + \overline{Y}$	$X + Y$	Q
0	0					
1	0					
0	1					
1	1					

- (b) Complete Figure 6.1 to show how a logic circuit can be constructed from two NOT gates, two OR gates and one AND gate to represent the Boolean equation above.

[9]

X ○ ———

————○ Q

Y ○ ———

Figure 6.1: Part of a logic circuit.

- (c) State which single logic gate has the same function as the complete circuit above.

[1]

END OF EXAMINATION