

BINDURA UNIVERSITY OF SCIENCE EDUCATION

FACULTY OF SCIENCE AND ENGINEERING

DEPARTMENT: ENGINEERING AND PHYSICS

PROGRAMME HBScED PHYSICS

COURSE CODE PH306 (1): ELECTRONICS 2

DURATION: 3 HOURS TOTAL MARKS: 100

JUN 2025

INSTRUCTIONS TO CANDIDATES

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

SECTION A

- 1 (a) Briefly describe the following states of a transistor.
- (i) cut-off. [1]
(ii) saturation. [2]
- (b) In a certain transistor, the transistor currents are given as $I_C = 10 \text{ mA}$ and $I_B = 70 \mu\text{A}$. Calculate I_E , α and β for this transistor. [6]
- (c) An operational amplifier can be used as a differentiator. Derive its output voltage. [5]
- (d) A sinusoidal voltage of peak value $10 \mu\text{V}$ and frequency of 2 kHz is applied as an input to an op-amp differentiator circuit. The values of the differentiating components are given as $R = 40 \text{ k}\Omega$ and $C = 3 \mu\text{F}$. Determine the output voltage. [4]
- (e) Prove the following expression using Boolean algebra:
- $$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC = AB + BC + AC$$
- [6]
- (f) Determine the truth table for the circuit shown in Fig. 1.1 [4]

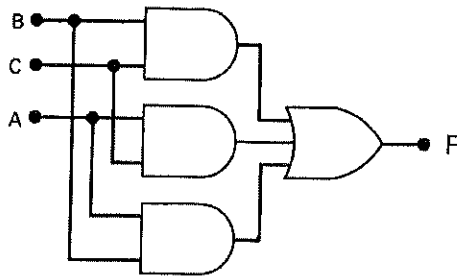


Fig. 1.1

- (g) Construct a circuit that is equivalent to an EX-NOR gate using NAND gates only. [6]
- (h) (i) What is meant by flip-flop? [2]
(ii) With the aid of a clearly labeled diagram, describe the operation of any one type of flip-flop. [4]

SECTION B

- 2 Consider the circuit shown in Fig. 2.1.

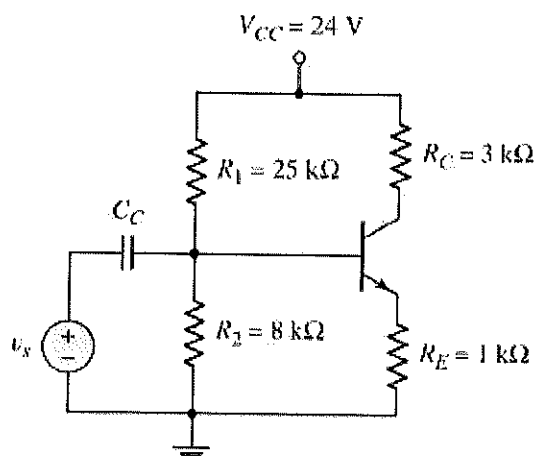


Fig. 2.1

Assuming $V_{BE(on)} = 0.7 \text{ V}$, determine I_{BQ} , I_{CQ} and V_{CEQ} for:

- (a) $\beta = 75$. [10]
(b) $\beta = 150$. [10]

- 3 (a) (i) Give any four characteristics of a real operational amplifier. [4]
(ii) Show that negative feedback reduces the gain of an operational amplifier. [5]
- (b) (i) Explain what is meant by null-offset in operational amplifiers. [2]
(ii) Describe how null-offset is corrected. [3]

(c) Fig. 3.1 shows an op-amp circuit.

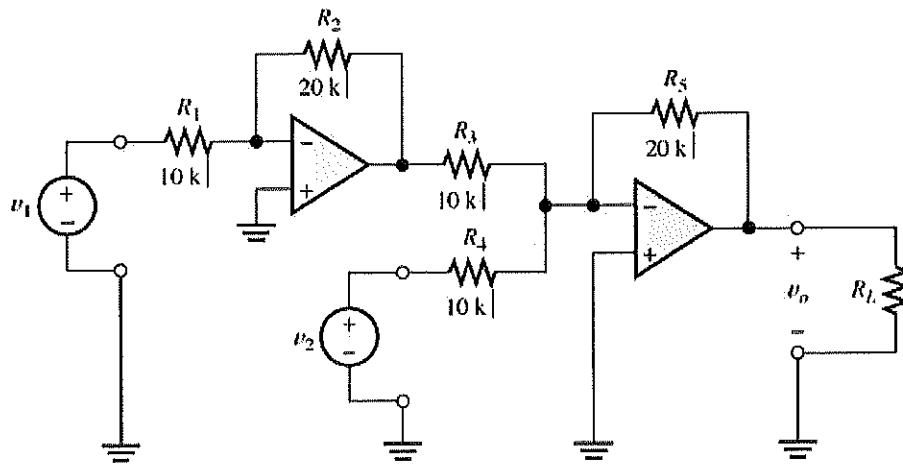


Fig. 3.1

Show that $v_o = 4v_1 - 2v_2$

[6]

- 4 An operational amplifier is connected in the circuit shown in Fig. 4.1. The switch S is open, the inverting input is at 0 V and the output voltage is $+V_o$.

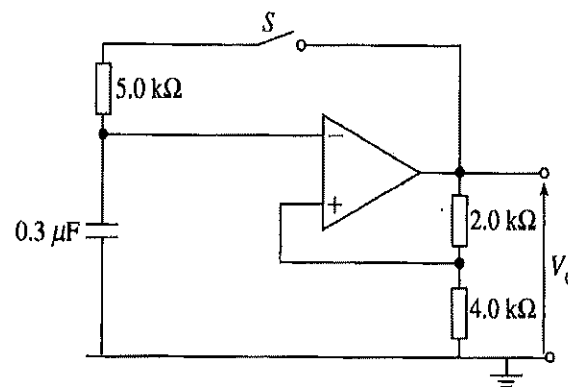


Fig. 4.1

- (a) Find the potential at the non-inverting input in terms of V_o . [3]
- (b) The switch S is then closed.
 - (i) Explain why the potential of the inverting input becomes progressively more positive. [3]
 - (ii) Calculate the time taken for the potential of the inverting input to reach the same potential as the non-inverting input. [4]
 - (iii) With the aid of graphs, describe and explain the subsequent variations in V_o . [10]

- 5 (a) Fig. 5.1 shows a logic circuit. Its truth table (incomplete) is shown in Table 5.1.

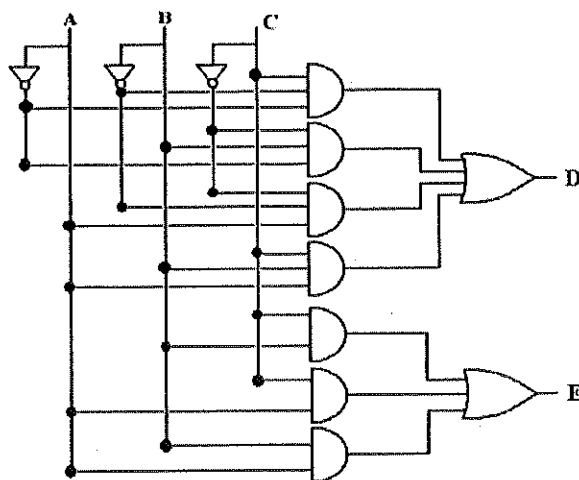


Fig. 5.1

Table 5.1

Input			Output	
A	B	C	D	E
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Copy and complete Table 5.1.

[20]

- 6 The Table below is a truth table for a logic circuit.

Input A	Input B	Input C	Output Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

- (a) Derive the Boolean function for the output Q. [5]
 (b) Draw the logic circuit that produces the output Q in (a). [5]
 (c) Hence, draw another circuit to show how the same output Q can be obtained using only two NOT gates, two AND gates and one OR gate. [10]

END OF PAPER