

BINDURA UNIVERSITY OF SCIENCE EDUCATION

PHYSICS AND ENGINEERING DEPARTMENT

BSC (HONS) NETWORK ENGINEERING

PH206: ELECTRONICS 1

MAR 2023

TIME: 3 HOURS

INSTRUCTIONS

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

Physical constants

Electronic charge, $e = 1.6 \times 10^{-19} \text{ C}$

Boltzmann's constant, $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$

SECTION A

1 (a) Define the following as regards to semiconductor diodes:

(i) Biasing of diode.

[2]

(ii) Forward voltage.

[2]

(iii) Reverse voltage.

[2]

(b) The ideal diode current equation relating the voltage V and current I is given by:

$$I = I_s \left[e^{(V/\eta V_T)} - 1 \right]$$

where symbols have their usual meanings.

(i) Define the remaining symbols in the equation.

[3]

(ii) Calculate V_T at 298 K.

[3]

(c) A bipolar junction transistor (BJT) function is usually considered in terms of currents: a relatively small current through one of the transistor's terminals exerts control over a much larger current. Fig. 1.1 shows two transistors.

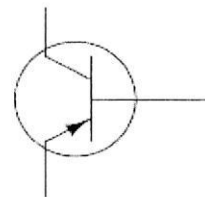
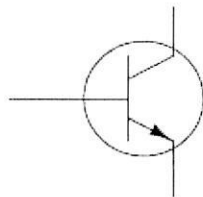


Fig. 1.1

Redraw Fig. 1.1 and

- (i) Identify the NPN and PNP transistor and explain the difference between the two. [6]
- (ii) Indicate the directions of all currents for these two transistors, clearly identifying which of the currents is doing the control, and which of the currents is being controlled: [6]
- (d) Calculate I_E in a transistor for which $\beta = 50$ and $I_B = 20 \mu A$. [4]
- (e) In a common base connection, current amplification factor is 0.9. If the emitter current is 1mA, determine the value of base current. [6]
- (f) What is meant by the CMRR of an operational amplifier? [2]
- (g) What are differential gain and common-mode gain of a differential amplifier? [4]

SECTION B

- 2 Determine the currents I_1 , I_2 and I_3 for the network shown in Fig. 2.1. [20]

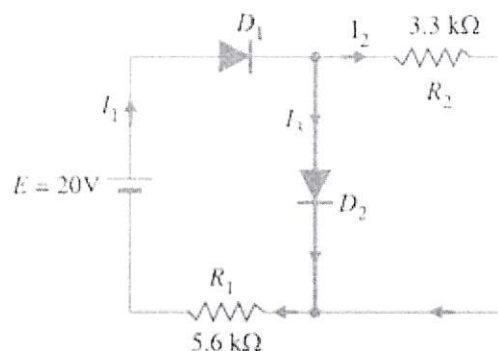


Fig. 2.1

- 3 Find the current through the diode in the circuit shown in Fig. 3.1. Assume the diode to be ideal. [20]

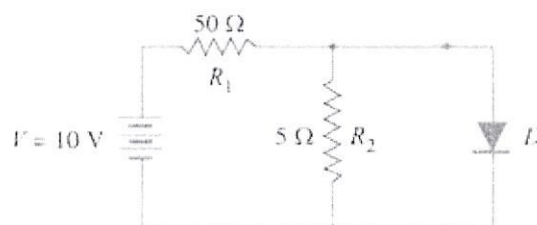


Fig. 3.1

- 4 Determine I_B , V_{CE} and V_{CB} in the transistor circuit shown in Fig. 4.1. The transistor is of silicon and has $\beta = 150$. [20]

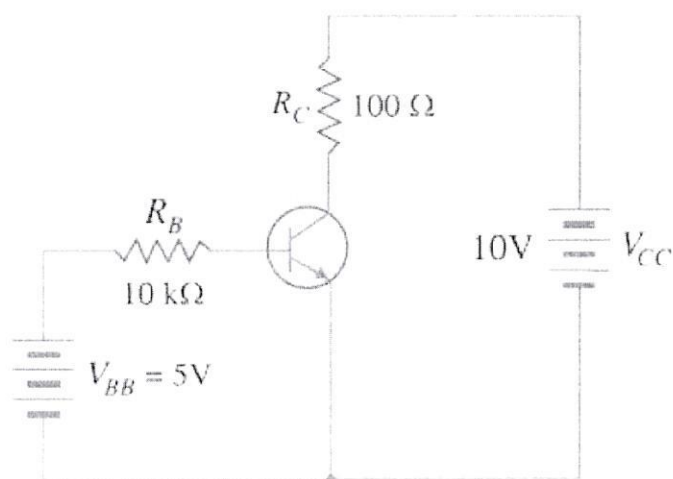


Fig. 4.1

- 5 Determine the Q point of the transistor circuit shown in Fig. 5.1. Also draw the d.c. load line. You are given that $\beta = 200$ and $V_{BE} = 0.7$ V. [20]

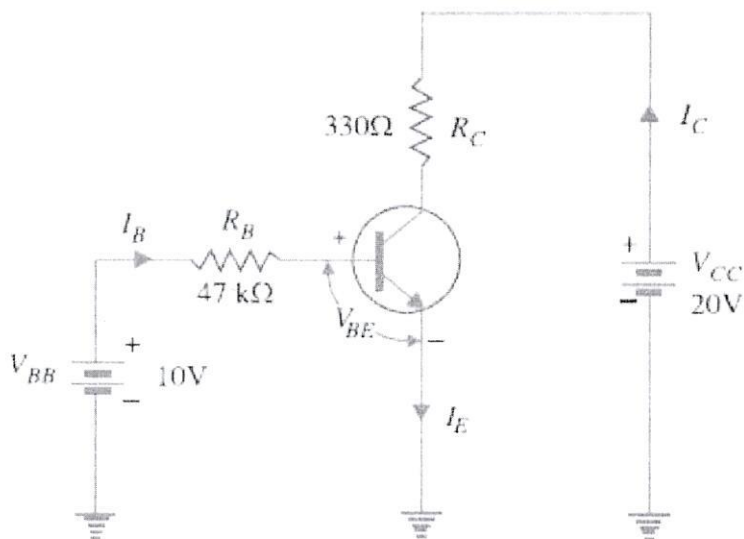


Fig. 5.1

- 6 (a) Give any four characteristics of an ideal operational amplifier. [4]
- (b) Fig. 6.1 shows an op-amp circuit.

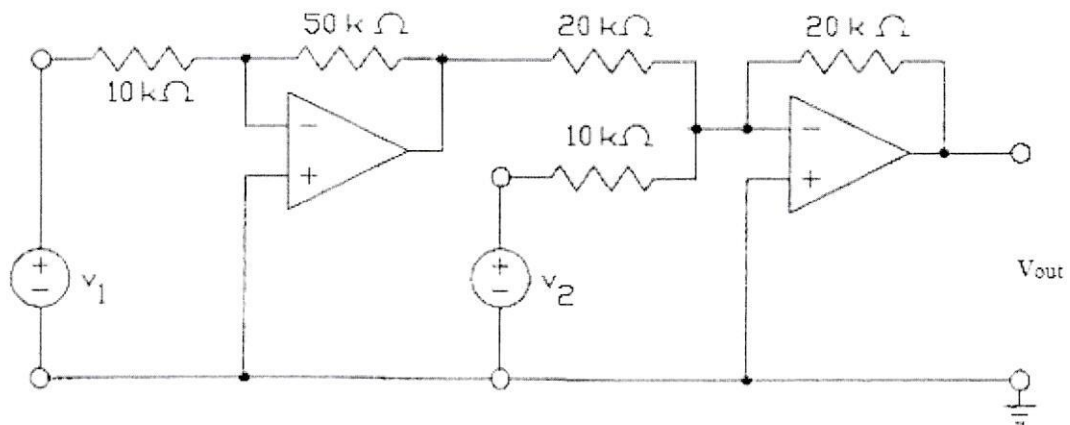


Fig. 6.1

- (i) Obtain an expression of v_{out} in terms of v_1 and v_2 . [13]
- (ii) Hence calculate the value of v_{out} when $v_1 = 500$ mV and $v_2 = 25$ mV. [3]

END OF EXAMINATION