

**BINDURA UNIVERSITY OF SCIENCE EDUCATION**

**FACULTY OF SCIENCE AND ENGINEERING**

**DEPARTMENT: ENGINEERING AND PHYSICS**

**PROGRAMME BSc HONOURS DEGREE IN COMPUTER SCIENCE / BSc EDUCATION HONOURS  
DEGREE IN COMPUTER SCIENCE**

**COURSE CODE PH206 (1): ELECTRONICS 1**

**DURATION: 3 HOURS      TOTAL MARKS: 100**

**INSTRUCTIONS TO CANDIDATES**

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

**SECTION A**

- 1 (a) Convert the following from rectangular to polar form:  $F = 4 + j3$ . [4]
- (b) Determine the sum of  $F_1 = 6 + j2$  and  $F_2 = 5 + j6$ . [4]
- (c) Find the product of  $F_1$  and  $F_2$  if  $F_1 = 6 + j4$  and  $F_2 = 3 + j9$ . [4]
- (d) Given that  $F_1 = 3 \angle 80^\circ$  and  $F_2 = 12 \angle 20^\circ$ , calculate the product of  $F_1$  and  $F_2$ . [4]
- (e) Transform the following sinusoid in time domain to phasor domain:  $V = 10\cos(70t - 20^\circ)$  V. [5]
- (f) Convert the sinusoid corresponding to the following phasor to time domain:  $I = -14 \angle 60^\circ$  A. [5]
- (g) The instantaneous current of an ac sinusoidal current is given by  $= I_m \cos \omega t$ . Show that  $I_{rms} = \frac{I_m}{\sqrt{2}}$ . [6]
- (h) Distinguish between ideal and practical sources in electric circuit theory. [2]
- (i) Use resistor colour codes to determine the resistances of resistors with the following band colours:
  - (1) green, brown, blue, silver. [2]
  - (2) yellow, violet, silver. [2]
  - (3) grey, red, gold. [2]

## SECTION B

- 2 (a) Using the Wye-Delta transformation, find the equivalent resistance between J and K in Fig. 2.1. [18]

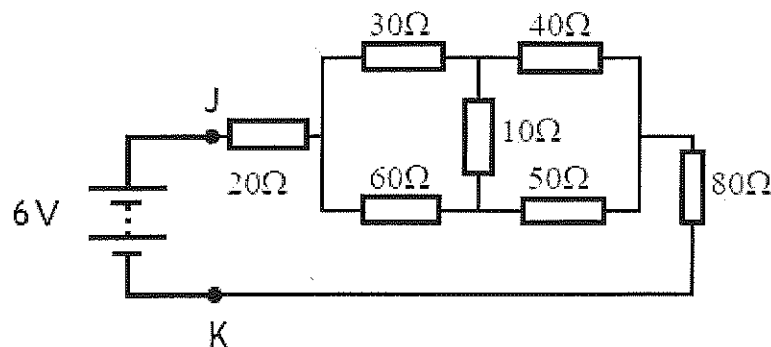


Fig. 2.1

- (b) Use your answer in (a) to determine the value of the current supplied by the power source. [2]
- 3 (a) Using the Superposition Theorem, determine the current through the  $1\ \Omega$  resistor in the circuit in Fig. 3.1. [16]

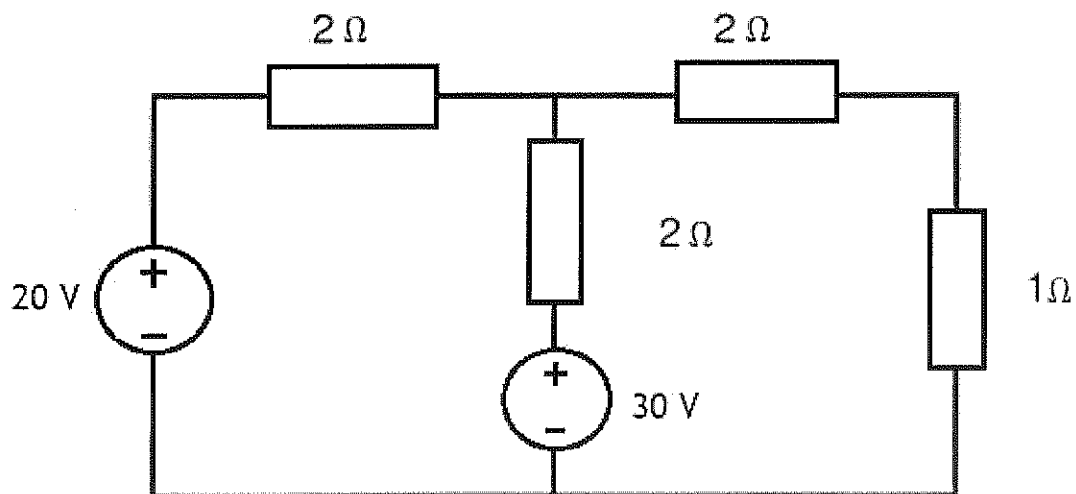


Fig. 3.1

- (b) Calculate the amount of heat energy dissipated in the  $1\ \Omega$  resistor in part (a) over a time interval of 1 hour. [4]

4

Use Thevenin's Theorem to find the Thevenin voltage ( $V_{TH}$ ), Thevenin resistance ( $R_{TH}$ ) and the load current  $I_L$  flowing through and load voltage ( $V_L$ ) across the load Resistor  $R_L = 5\text{ k}\Omega$  in the network of Fig. 4.1. [20]

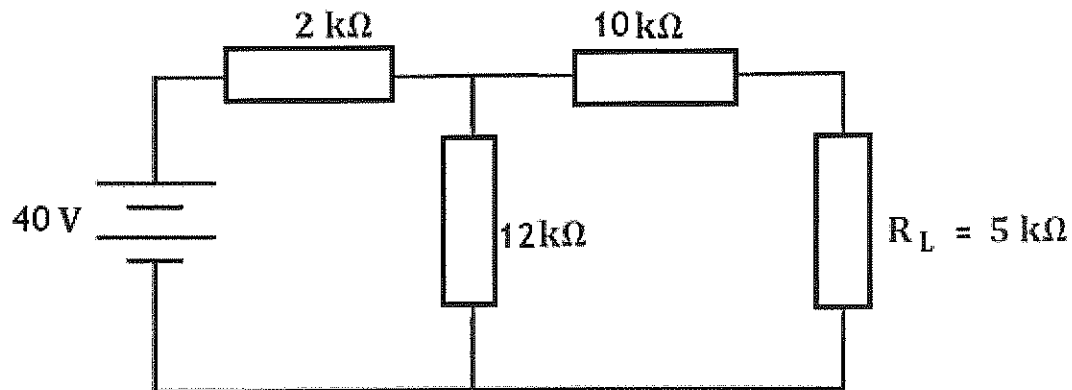


Fig. 4.1

5

Find the Norton current ( $I_N$ ), Norton resistance ( $R_N$ ) and the load current  $I_L$  flowing through and load voltage ( $V_L$ ) across the load resistor  $R_L = 15\text{ }\Omega$  using Norton's Theorem in the network of Fig. 5.1. [20]

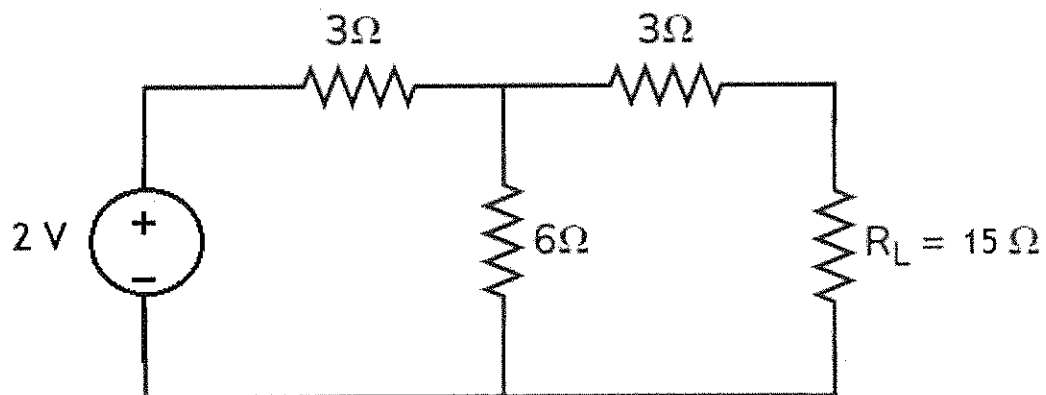


Fig. 5.1

6

A current waveform is described by the function:  $i(t) = \begin{cases} 5t, & 0 < t < 2 \\ -10, & 2 < t < 4 \end{cases}$  as shown in Fig. 6.1.

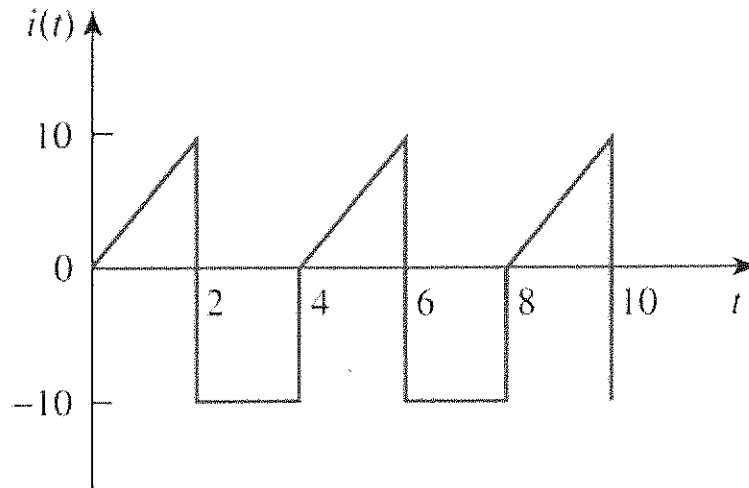


Fig. 6.1

The current is passed through a  $2\text{-}\Omega$  resistor.

- (a) Find the rms value of the current. [18]
- (b) Calculate the average power absorbed by the resistor. [2]