

**BINDURA UNIVERSITY OF SCIENCE EDUCATION**  
**FACULTY OF SCIENCE EDUCATION**  
**DEPARTMENT OF MATHEMATICS AND SCIENCE EDUCATION**  
**PHE107: PHYSICS FOR COMPUTER SCIENCE**  
**TIME: 3 HOURS**

**INSTRUCTIONS**

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

**Physical constants**

Electronic charge,  $e = 1.6 \times 10^{-19} \text{ C}$   
 Boltzmann's constant,  $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$   
 Mass of an electron,  $m_e = 9.11 \times 10^{-31} \text{ kg}$   
 Permittivity of free space,  $\epsilon_0 = 8.85 \times 10^{-12} \text{ Fm}^{-1}$   
 Permeability of free space,  $\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$   
 Velocity of light in vacuum,  $c = 3.00 \times 10^8 \text{ ms}^{-1}$   
 Universal Gravitational Constant,  $G = 6.7 \times 10^{-11} \text{ Nm}^2\text{kg}^{-2}$   
 Acceleration due to gravity,  $g = 9.81 \text{ ms}^{-2}$   
 Electric potential at infinity,  $V_\infty = 0$

**AUG 2024**

**SECTION A**

**QUESTION 1**

- (a) Calculate the angle between the vectors  $\vec{r} = (2, 2, 5)$  and  $\vec{s} = (-2, -4, 1)$ . [4]
- (b) Distinguish between a dot product and a cross product of vectors? [2]
- (c) Calculate the cross product of the vectors  $\vec{p} = (1, 3, 5)$  and  $\vec{q} = (-2, 2, 1)$ . [5]
- (d) Verify that the cross product calculated in (c) is orthogonal to both  $\vec{p}$  and  $\vec{q}$ . [2]
- (e) An object moves at  $5 \text{ ms}^{-1}$  around a circular path of radius  $15 \text{ m}$ . Determine the centripetal force. [3]
- (f) Calculate the magnitude of the electric field at a point  $2 \times 10^{-7} \text{ m}$  from a proton. [3]
- (g) A  $120 \mu\text{F}$  capacitor is charged to a p.d. of  $10 \text{ V}$ . Calculate the charge acquired by the capacitor. [2]
- (h) A student has available some resistors, each of resistance  $100 \Omega$ . Draw circuit diagrams, one in each case, to show how a number of these resistors may be connected to produce a combined resistance of; (1)  $200 \Omega$  (2)  $50 \Omega$  (3)  $40 \Omega$  [6]
- (i) A charged particle carrying twice the magnitude of the basic charge moves with velocity  $\vec{v} = 2\vec{i} - 3\vec{j} + \vec{k} \text{ ms}^{-1}$  in a region where the magnetic field is  $\vec{B} = 3\vec{i} + \vec{j} + 4\vec{k} \text{ T}$ .
  - i. Calculate the magnitude of the magnetic force  $\vec{F}$  on this particle. [5]
  - ii. Verify that  $\vec{F}$  is centripetal in nature. [3]
- (j) What do you understand by inductive reactance? [1]
- (k) A resistor of resistance  $30 \Omega$  is connected in series with an inductor of inductive reactance  $15 \Omega$  and a  $240 \text{ V}$  supply. Calculate the current flowing in the circuit. [4]

### SECTION B

- 2 (a) A particle is moving in three dimensions. Its position vector is given by;  

$$\mathbf{r} = 2\hat{x} + (4 + t)\hat{y} - (2 + 3t - 3t^2)\hat{z}.$$
 Distances are in metres and the time  $t$  in seconds.
- (i) What is the velocity vector at  $t = +5$ ? [3]  
 (ii) Evaluate the speed in  $\text{ms}^{-1}$  at  $t = +5$ . [3]  
 (iii) Determine the acceleration vector and its magnitude in  $\text{ms}^{-2}$  at  $t = +5$ . [6]  
 (b) Find the resultant and direction of the forces given in Figure 1. [8]

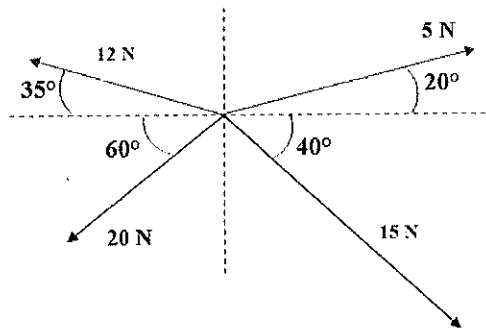


Figure 1

- 3 Figure 2 shows a system of charges located at the corners of a rectangle in vacuum. It is given that  $q_1 = 6.00 \times 10^{-9} \text{ C}$ ,  $q_2 = -2.00 \times 10^{-9} \text{ C}$  and  $q_3 = 5.00 \times 10^{-9} \text{ C}$ .

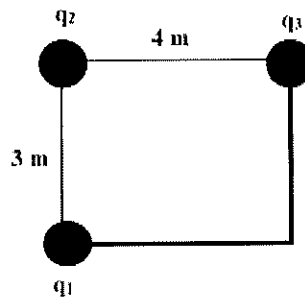


Figure 2

- Calculate the electric potential at the corner where there is no charge. [20]
- 4 Figure 3 shows a circuit containing two voltage sources and some resistors.

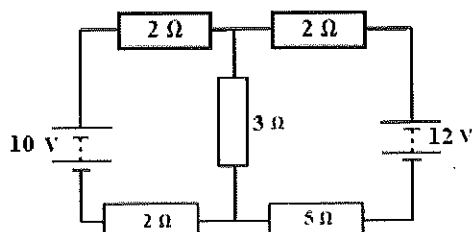


Figure 3

- (a) Use Kirchhoff's rules to determine the current passing through the  $3 \Omega$  resistor. [18]

- 5 (b) Hence calculate the potential difference across the  $3\ \Omega$  resistor. [2]  
Figure 4 shows a network of capacitors connected to a  $60\text{ V}$  battery.

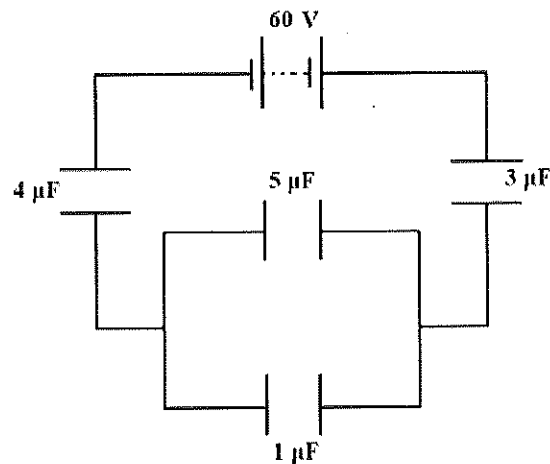


Figure 4

- Calculate
- the equivalent capacitance of the capacitors. [5]
  - the charge on each capacitor. [5]
  - the potential difference across each capacitor. [5]
  - the energy stored in each capacitor. [5]
- 6 An inductor of inductive reactance  $40\ \Omega$  and a capacitor of capacitive reactance  $10\ \Omega$  are connected in series with a  $220\text{ V}$  a.c. generator.
- Draw a circuit diagram showing how the components are connected. [5]
  - Draw the phasor diagram for  $V_L$  and  $V_C$ . [4]
  - Calculate the following.
    - impedance [3]
    - total current [2]
    - potential drop across the inductor [2]
    - potential drop across the capacitor [2]
    - the phase angle [2]

END OF EXAMINATION