

BINDURA UNIVERSITY OF SCIENCE EDUCATION

FACULTY OF ENGINEERING AND SCIENCES

DEPARTMENT OF ENGINEERING AND PHYSICS

ELECTRONIC ENGINEERING CIRCUITS

EEE 1203

9 - JUN 2023

Examination Paper [3]

This examination paper consists of 8 pages

Time Allowed: 3 hours

Total Marks: 100

Special Requirements: Calculator, Graph Paper

Examiner's Name: S. Komichi

INSTRUCTIONS

1. Answer any FIVE questions only.
2. Each question carries 20 marks.
3. Show your steps clearly in any calculation.
4. Start the answers for each question on a fresh page.

MARK ALLOCATION

QUESTION	MARKS
1.	20
2.	20
3.	20
4.	20
5.	20
6.	20
7.	20
TOTAL	100

Page 1 of 8

Question 1

For the characteristics of Figure. 1.1 below;

- Determine the ac resistance at $I_D = 2 \text{ mA}$.
- Determine the ac resistance at $I_D = 25 \text{ mA}$.
- Compare the results of parts (a) and (b) to the dc resistances at each current level.

[3], [3], [3]

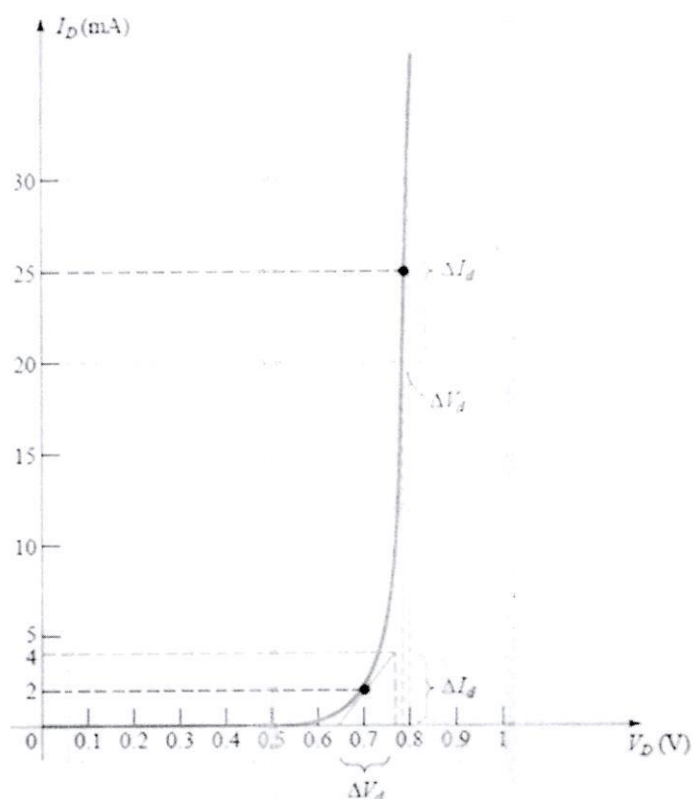


Figure 1.1 Diode Characteristics

- Determine I_D , V_{D2} , and V_o for the circuit of Figure 1.2 below;

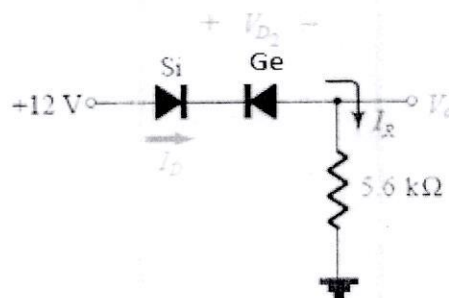


Figure 1.2: Diode Circuit

[7]

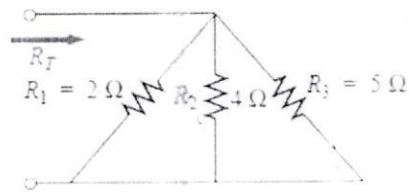


Figure 1.3: Resistor Network

(d) (ii) Determine the total resistance for the network of Figure 1.3 above. [4]

Question 2

a) For the series diode reverse configuration of Figure 2.1, determine V_D , V_R , and I_D . [2], [2], [4].

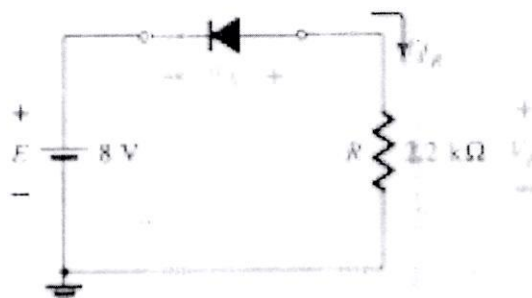


Figure 2.1: Series Diode

b) Determine V_D and I_D for the series circuit of Figure 2.2 below.

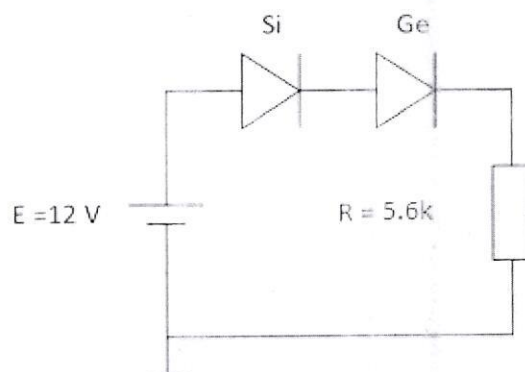


Figure 2.2: Diodes Network

[3], [3]

- c) (i) Find the voltages V_1 , V_3 , and V_{ab} for the network of Figure 2.3 below.
- (ii) Calculate the source current I_s .

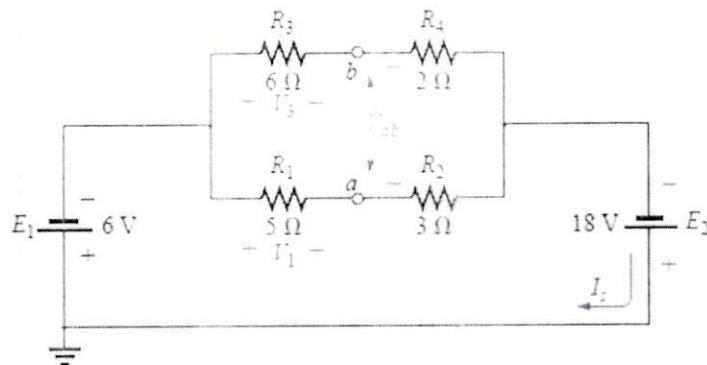


Figure 2.3: Resistor Network [3], [3]

Question 3

- a) The emf of a battery is 22.5V. How much charge flows if energy transferred is 90J? What is the current if the transfer time is 1.5 minutes? [5]
- b) Determine the resistance of a 30m copper wire with a diameter of 0.032cm and resistivity of 1.723×10^{-8} . [5]
- c) What is the pd across a lamp that dissipates 1000J in 10 seconds if current is 0.4A? [5]
- d) Draw the common collector transistor configuration circuit clearly showing the current directions. [5]

Question 4

- a) Calculate the indicated currents (I_5 , I_s , I_6) and voltages (V_5 across R_5 , V_7 across R_7) of Figure 4.1 below. [2], [2], [2], [2], [2]

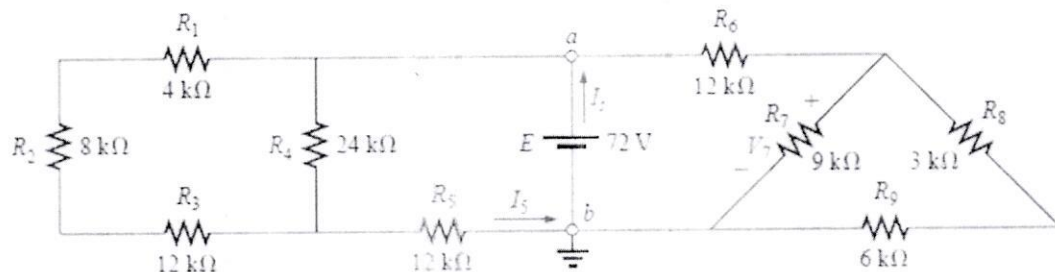


Figure 4.1: Resistor Networks

- b) Determine the voltage V_o for the network of Figure 4.2 below. [5]

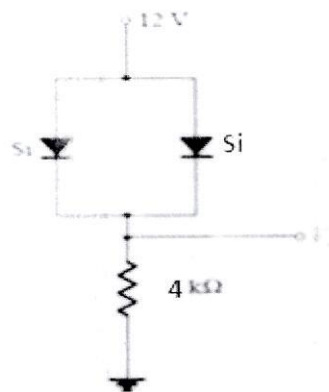


Figure 4.2: Diode Network

- c) Draw the common emitter transistor configuration circuit clearly showing the current directions. [5]

Question 5

a) Determine I_s , I_{R2} , I_{R3} , I_{R4} , I_{R5} , I_{R6} and R_T for the circuit in Figure 5.1 below;

[2], [2], [1], [1], [1], [1], [2]

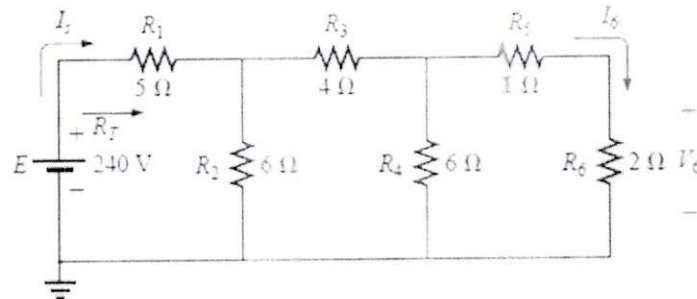


Figure 5.1: Resistor Network

b) For the emitter bias network of Figure 5.2 below, determine:

- (i) I_B .
- (ii) I_C .
- (iii) V_{CE} .
- (iv) V_C .
- (v) V_E .
- (vi) V_B .

[2], [1], [2], [2], [2], [1]

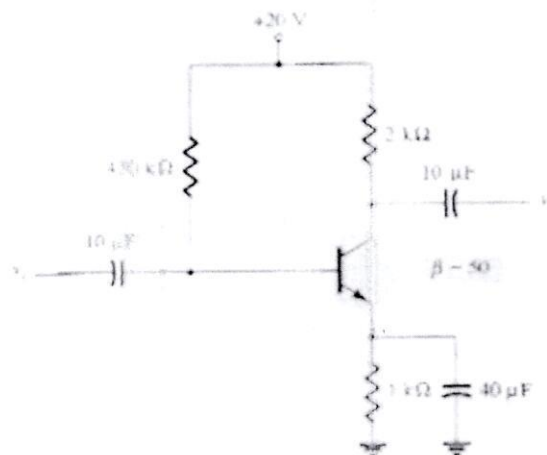


Figure 5.2: Emitter Stabilized Circuit

Question 6

a) Determine the currents I_1 , I_2 , and I_{D2} for the network of Figure 6.1 below.

[3], [3], [3]

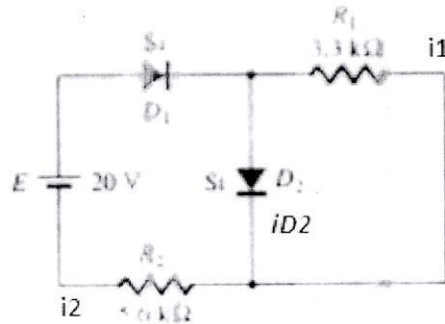


Figure 6.1: Resistor-Diode Network

- b) (i) For the network of Figure 6.2 below, determine the range of R_L and I_L that will result in V_{RL} being maintained at 10 V.
- (ii) Determine the maximum and minimum wattage rating of the diode in Figure 6.2 below.

[4], [4], [3]

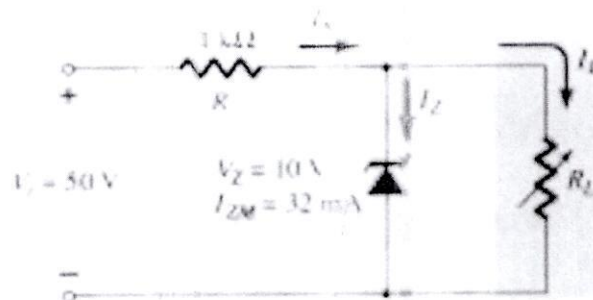


Figure 6.2: Zener Regulator

Question 7

- a) For the Zener diode network of Figure 7.1 below, determine V_L , V_R , I_Z , and P_Z . Repeat with $R_L = 3 \text{ k}\Omega$. [5], [5]

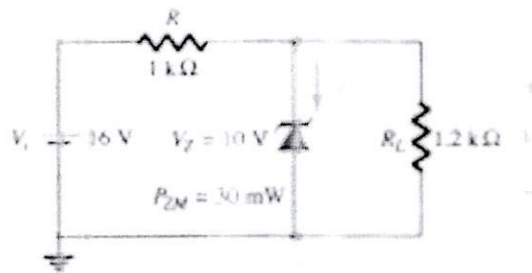


Figure 7.1: Bias Network

Question 7

- b) Determine the dc bias voltage V_{CE} and the current I_C for the voltage-divider configuration of Figure 7.2 below. [10]

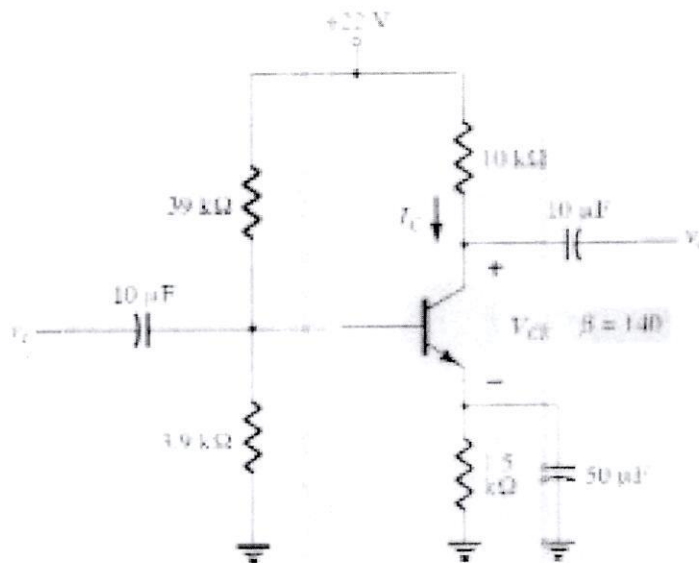


Figure 7.2: Voltage Divider Circuit