

# BINDURA UNIVERSITY OF SCIENCE EDUCATION

## PHYSICS AND ENGINEERING DEPARTMENT

### PH206: ELECTRONICS I

TIME: 3 HOURS

 AUG 2023

#### INSTRUCTIONS

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

#### SECTION A

- 1 (a) What is the difference between ideal and practical sources of electricity. [2]
- (b) Colour bands are important in determining the sizes of carbon resistors. Determine the sizes of resistors with the following band colours:
- (i) green, brown, blue, silver. [2]  
(ii) yellow, violet, silver. [2]  
(iii) grey, red, gold. [2]
- (c) For an ideal diode, the net current flowing through the diode is related to the voltage  $V$  applied across the diode terminals as follows:
- $$I = I_0 \left( e^{\frac{qV}{kT}} - 1 \right)$$
- where symbols have their usual meanings.
- (i) Define the symbols used. [3]  
(ii) Calculate the thermal voltage across the diode at 298 K. ( $k = 1.38 \times 10^{-23} \text{ J K}^{-1}$ ). [3]
- (d) State any four major properties of ideal operational amplifiers. [4]
- (e) The instantaneous current of an ac sinusoidal current is given by  $I = I_m \cos \omega t$ . Show that  $I_{rms} = \frac{I_m}{\sqrt{2}}$ . [6]
- (f) An alternating voltage signal is represented by  $v = 30 \sin 150\pi t$ . What is the frequency of the voltage signal? [6]
- (g) A 2.0 H inductor and a 30  $\Omega$  resistor are connected in series with an a.c. voltage source. The voltage across the inductor is given as  $v = 100 \sin 20t$ . Determine the root mean square value of the applied voltage. [6]

- (h) Calculate the frequency at which an inductor of  $50\text{ mH}$  has the same reactance as a capacitor of  $470\text{ }\mu\text{F}$ . [4]

### SECTION B

- 2 Using the Wye-Delta transformation, obtain the equivalent resistance  $R_{ab}$  and find the current  $i$  for the circuit in Fig. 2.1. [20]

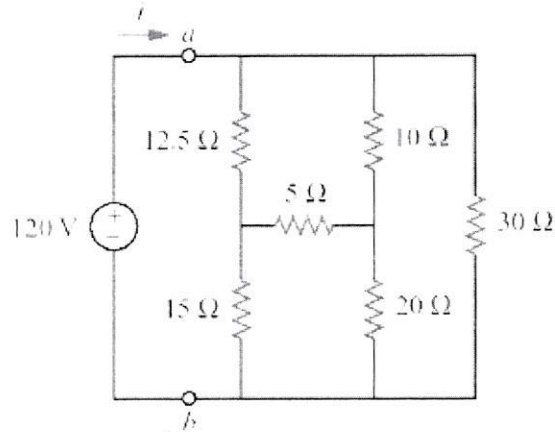


Fig. 2.1

- 3 (a) Determine the current through AB in the circuit in Fig. 3.1 using Norton's theorem. [16]

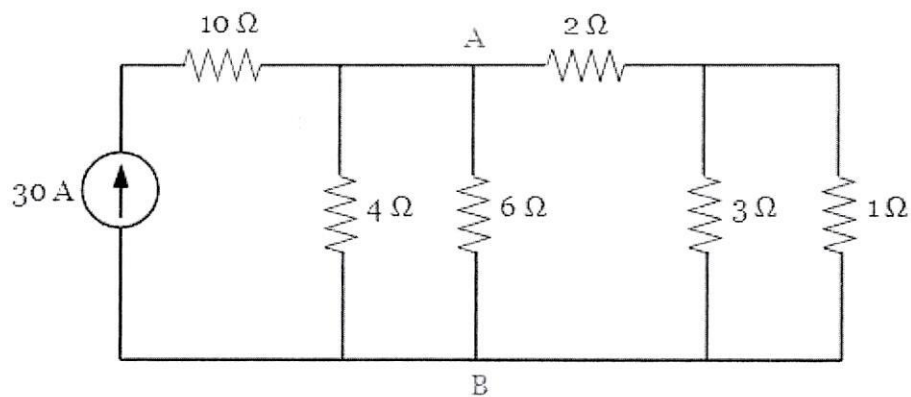


Fig. 3.1

- (b) Calculate the amount of heat energy dissipated in the  $6\text{ }\Omega$  resistor in part (a) over a time interval of 1 hour. [4]

- 4 (a) Solve the circuit in Fig. 4.1 to find the current through  $15\ \Omega$  using Thevenin's Theorem. [16]

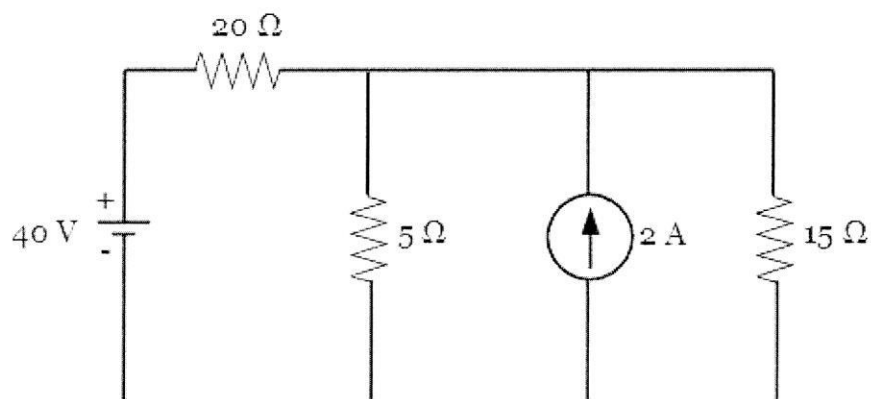


Fig. 4.1

- (b) Calculate the potential difference across and the power dissipated in the  $15\ \Omega$  resistor in part (a). [4]
- 5 (a) State the superposition theorem as applied to d.c. circuit analysis. In applying this theorem, how does one set voltage and current sources to zero? [4]
- (b) Fig. 1 shows an electric circuit containing two voltage sources and some resistors.

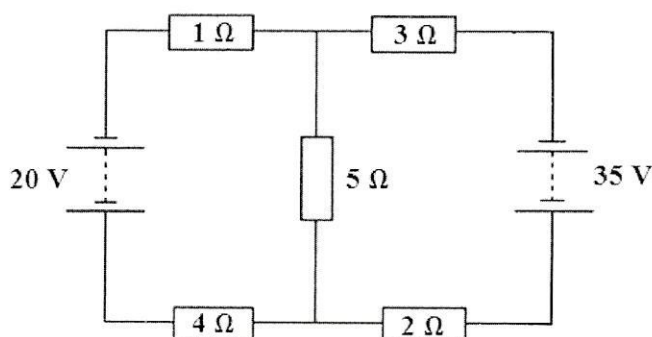


Fig. 5.1

- (i) Use the superposition theorem to determine the value of the current through the  $5\ \Omega$  resistor. [15]
- (ii) State the direction of flow of this current (upwards or downwards in this resistor). [1]

- 6 A current waveform is described by the function:  $i(t) = \begin{cases} 5t, & 0 < t < 2 \\ -10, & 2 < t < 4 \end{cases}$  as shown in Fig. 6.1.

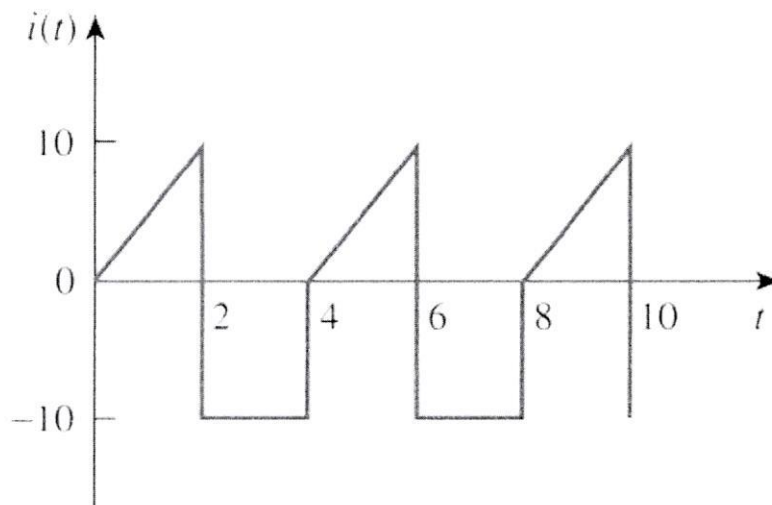


Fig. 6.1

The current is passed through a  $2\text{-}\Omega$  resistor.

- (a) Find the rms value of the current. [18]
- (b) Calculate the average power absorbed by the resistor. [2]