

BINDURA UNIVERSITY OF SCIENCE EDUCATION
FACULTY OF SCIENCE AND ENGINEERING
DEPARTMENT OF ENGINEERING AND PHYSICS
DIGITAL ELECTRONICS
EEE1207

Examination Paper

This examination paper consists of 5 pages.

Time Allowed: 3 hours.

Total marks: 100

Special requirements: Non programmable scientific calculator

INSTRUCTIONS


1. Answer 5 questions only.
2. Each question carries 20 marks.
3. Show your steps clearly in any calculation.
4. Start the answers for each question on a fresh page.

MARK ALLOCATION

QUESTION	MARKS
1.	20
2.	20
3.	20
4.	20
5.	20
6.	20
TOTAL	100

QUESTION 1

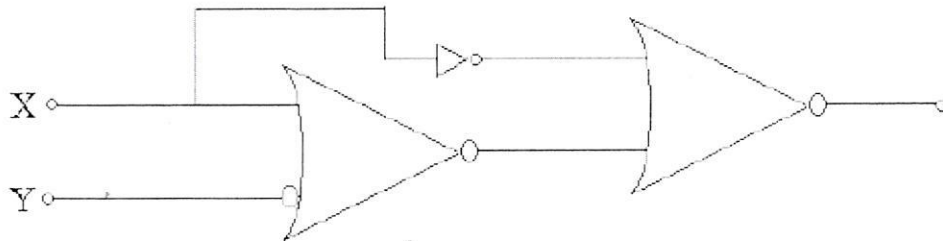- a) The logic circuit shown in the given fig.2 below can be minimised to what? [4]



- b) Perform 2's complement subtraction of $7 - 10$ (noted the numbers are in base 10) [3]
- c) Simplify the Boolean expression $F = C(B + C)(A + B + C)$. [4]
- d) Determine the binary numbers represented by the following decimal numbers. (6)
- (i) 25.5
 - (ii) 10.625
 - (iii) 0.6875
- e) Convert 2222 in Hexadecimal number. [3]

QUESTION 2

- a) Simplify the following expression into sum of products using Karnaugh map $F(A,B,C,D) = \Sigma(1,3,4,5,6,7,9,12,13)$. [7]
- b) Give the details of excess 3 code and gray code using 4-binary digits. Compare the two codes. [7]
- c) What is a flip-flop? Briefly state the difference between a Latch and a flip-flop, stating the application of a flip-flop. [5]
- d) What is the decimal equivalent of hex number A5? [1]

QUESTION 3

- a) Simplify and draw the logic diagram for the given expression

$$F = \overline{A}BC + \overline{A}B\overline{C} + \overline{A}B\overline{C} + A\overline{B}C + A\overline{B}C \quad [7]$$

- b) Discuss the difference between a demultiplexer and a decoder. [4]

- c) Add 648 and 487 in BCD code. [3]

- d) Give the truth table of S-R and D-flip-flops. Convert the given S-R flip-flop to a D-flip-flop. [6]

QUESTION 4

- a) Prove the following Boolean identities. [4]

$$(i) XY + YZ + \overline{Y}Z = XY + Z$$

$$(ii) A.B + \overline{A}.B + \overline{A}.\overline{B} = \overline{A} + B$$

- b) Convert the following

i. 430 to Excess-3 code. [2]

ii. 10110 to Gray code. [2]

- c) What is a decoder? Draw the logic circuit of a 3 line to 8-line decoder and explain its working principle. [8]

- d) What are synchronous counters? [2]

- e) What are the advantages of a CMOS? [2]

QUESTION 5

- a) What is the octal equivalent of the decimal number 84? [2]
- b) Design a MOD-6 synchronous counter using J-K Flip-Flops. [7]
- c) What are the gates required to build a half adder and illustrate using a diagram? [6]
- d) Convert 3117 (decimal value) to hex, then from hex to binary. [3]
- e) Convert the following (BCD) 1001011110110101 to its decimal equivalent. [2]

QUESTION 6

- a) Design an 8 to 1 multiplexer by using the four variable function given by $F(A, B, C, D) = \sum m(0,1,3,4,8,9,15)$. [10]
- b) What is a shift register? What are its various types and list some of its applications? [6]
- c) What are the advantages of digital techniques over analogue techniques? [4]

THE END