

BINDURA UNIVERSITY OF SCIENCE EDUCATION

FACULTY OF SCIENCE AND ENGINEERING

DEPARTMENT: ENGINEERING AND PHYSICS

**PROGRAMME BSc HONOURS DEGREE IN COMPUTER SCIENCE / BSc EDUCATION HONOURS
DEGREE IN COMPUTER SCIENCE**

COURSE CODE PH107 (2): PHYSICS FOR COMPUTER SCIENCE

DURATION: 3 HOURS TOTAL MARKS: 100

JUN 2025

INSTRUCTIONS TO CANDIDATES

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

Physical constants

Electronic charge, $e = 1.6 \times 10^{-19} \text{ C}$
 Boltzmann's constant, $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$
 Mass of an electron, $m_e = 9.11 \times 10^{-31} \text{ kg}$
 Permittivity of free space, $\epsilon_0 = 8.85 \times 10^{-12} \text{ Fm}^{-1}$
 Permeability of free space, $\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$
 Velocity of light in vacuum, $c = 3.00 \times 10^8 \text{ ms}^{-1}$
 Universal Gravitational Constant, $G = 6.7 \times 10^{-11} \text{ Nm}^2\text{kg}^{-2}$
 Acceleration due to gravity, $g = 9.81 \text{ ms}^{-2}$
 Electric potential at infinity, $V_\infty = 0$

SECTION A

- 1 (a) It is given that \vec{L} and \vec{M} are such that $\vec{L} = \vec{i} - 3\vec{j} + 5\vec{k}$ and $\vec{M} = 3\vec{i} + 3\vec{j} - 4\vec{k}$. Find $\vec{L} \times \vec{M}$ and verify that this vector is orthogonal to both \vec{L} and \vec{M} . [6]
- (b) A van travelling at a velocity of 10 ms^{-1} accelerates uniformly for 5 s at a rate of 2.5 ms^{-2} . Calculate the distance travelled during this time. [3]
- (c) A positive charge of $+40 \mu\text{C}$ is fixed at the origin and another charge of $-20 \mu\text{C}$ is fixed to the x -axis at $x = 2 \text{ m}$. Find along the x -axis only one possible location where the electric field due to the two charges is zero. [6]
- (d) If 200 J is required to carry a 10 C charge from point P to point Q what is the potential difference between the two points? [2]

- (e) A $1500\ \mu\text{F}$ capacitor is charged to a p.d. of $25\ \text{V}$. Calculate the charge acquired by the capacitor. [2]
- (f) In an experiment to study capacitors, a capacitor of capacitance C discharges through a resistor of resistance R . Show that the time t when the charge on the capacitor become half of the initial value is given by $t = CR\ln 2$. [5]
- (g) A student has available some resistors, each of resistance $100\ \Omega$. Draw circuit diagrams, one in each case, to show how a number of these resistors may be connected to produce a combined resistance of;
- (1) $200\ \Omega$ (2) $50\ \Omega$ (3) $40\ \Omega$ [3]
- (h) A charged particle carrying twice the magnitude of the basic charge moves with velocity $\vec{v} = \vec{i} - 5\vec{j} + 2\vec{k}\ \text{ms}^{-1}$ in a region where the magnetic field is $\vec{B} = 4\vec{i} - \vec{j} - 6\vec{k}\ \text{T}$.
- (1) Calculate the magnitude of the magnetic force \vec{F} on this particle. [5]
 (2) Verify that \vec{F} is centripetal in nature. [3]
- (i) What do you understand by inductive reactance? [1]
- (j) A resistor of resistance $500\ \Omega$ is connected in series with an inductor of inductive reactance $150\ \Omega$ and a $230\ \text{V}$ supply. Calculate the current flowing in the circuit. [4]

SECTION B

- 2 (a) A particle is moving in two dimensions. Its position vector is given by;
- $$\vec{r} = (4 + 3t - 2t^2)\hat{x} + (5 + t)\hat{y}.$$
- Distances are in metres and the time t in seconds.
- (i) What is the velocity vector after 2 seconds. [3]
 (ii) Evaluate the speed in ms^{-1} after 2 seconds. [3]
 (iii) Determine the acceleration vector and its magnitude in ms^{-2} after 2 seconds. [6]
- (b) Find the resultant and direction of the forces given in Fig. 1. [8]

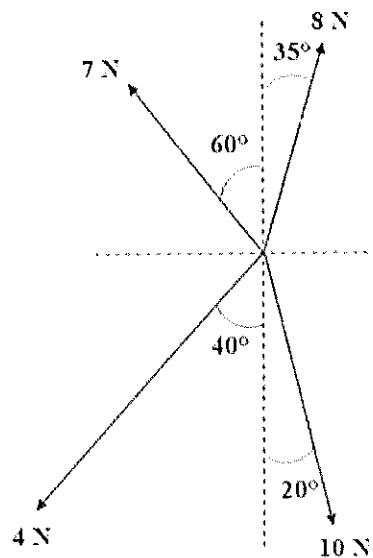


Fig. 1

- 3 Three point charges are located at the corners of an equilateral triangle as shown in Fig. 2.

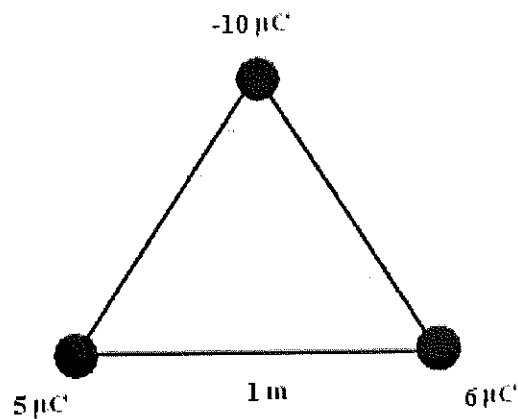


Fig. 2

- (a) Calculate the electric potential at the centre of the triangle. [18]
- (b) How much work is required to move a charge of $15 \mu\text{C}$ from infinity to the centre of the triangle? [2]

- 4 Fig. 3 shows a network containing two cells and some resistors.

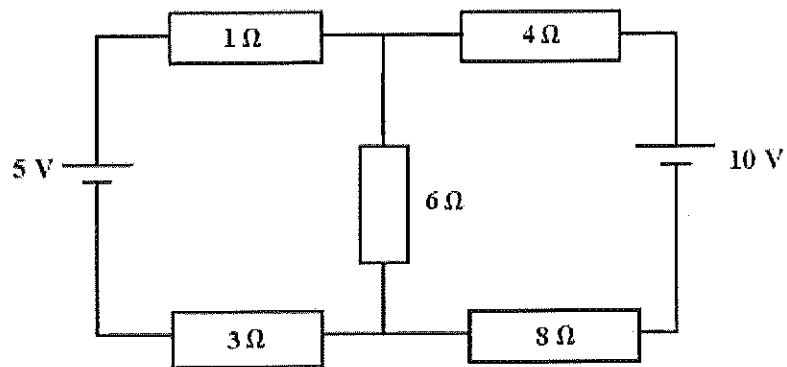


Fig. 3

- (a) Use Kirchhoff's rules to determine the value of the current through the $6\ \Omega$ resistor. [18]
- (b) Hence calculate the potential difference across the $6\ \Omega$ resistor. [2]

- 5 Fig. 4 shows a network of capacitors connected to a 20 V source.

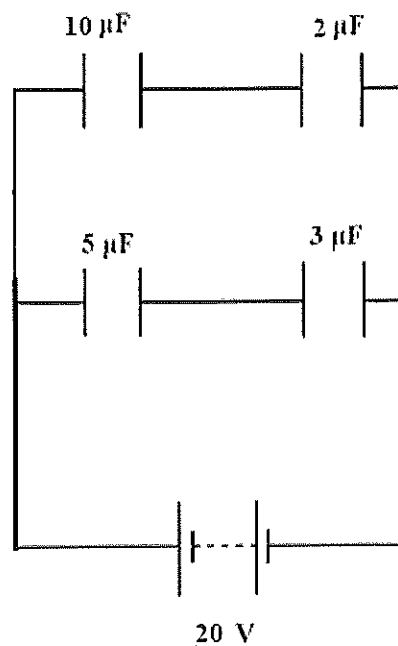


Fig. 4

Calculate

- (a) the equivalent capacitance of the capacitors. [5]
- (b) the charge on each capacitor. [5]
- (c) the potential difference across each capacitor. [5]
- (d) the energy stored in each capacitor. [5]

6 A resistor of resistance $60\ \Omega$ and a capacitor of capacitive reactance $80\ \Omega$ are connected in series with a 60 V a.c. generator.

- (a) Draw a circuit diagram showing how the components are connected. [5]
- (b) Draw the phasor diagram for V_R and V_C . [4]
- (c) Calculate the following.
 - (i) impedance [3]
 - (ii) total current [2]
 - (iii) potential drop across the resistor [2]
 - (iv) potential drop across the capacitor [2]
 - (v) the phase angle [2]