

BINDURA UNIVERSITY OF SCIENCE EDUCATION

FACULTY OF SCIENCE AND ENGINEERING

DEPARTMENT OF ENGINEERING AND PHYSICS

Bachelor of Science Honours Degree in Electronic Engineering

**EEE2202:**

**ELECTRONIC DRIVES**

**Duration: 3 hours**

**Total marks: 100**

#### INSTRUCTIONS

This paper contains seven questions each carrying 20 marks.

Answer any **FIVE** questions.

 **MAR 2023**

### Question 1

- a) (i) Highlight any two typical applications of the Schottky diode. [2]
- (ii) State any two advantages of the Schottky diode. [2]
- b) State the four types of transistor power losses, hence give a brief description of the losses. [8]
- c) Highlight any five different turn ON methods for the Silicon controlled rectifier. [5]
- d) State three advantages associated with the use of the stepper motor. [3]

### Question 2

- a) With the aid of a circuit diagram and supporting equations, describe the principle of operation of the Silicon Controlled Rectifier half-wave power control. [8]
- b) Briefly describe how thyristor protection is achieved. [5]
- c) With the aid of a circuit diagram, briefly describe the operation of the crowbar protection circuit. [7]

### Question 3

- a) With the aid of the Insulated-Gate Bipolar Transistor (IGBT) equivalent circuit diagram, describe its principle of operation. [8]
- b) (i) State the two classes of IGBTs. [2]
- c) Explain why the PT IGBTs cannot be as easily paralleled as MOSFETs, while the NPT IGBTs can be paralleled. [4]
- d) Briefly describe the three basic elements of the stepper motor system. [6]

#### Question 4


- a) (i) Describe the purpose served by the servomotor. [2]  
(ii) Hence highlight the components that constitute the servomotor. [3]
- b) (i) Draw the block diagram of the servo mechanism. [5]  
(ii) State the fundamental characteristics to be sought in any servo motor. [2]
- c) (i) Highlight any four advantages of DC servomotor. [4]  
(ii) Give any four typical applications of the DC servomotor. [4]

#### Question 5

- a) With the aid of a tree diagram, highlight the classifications of the stepper motor. [5]
- b) With the aid of a diagram/s, explain how the Linear Variable Differential Transformer (LVDT) is used to measure displacement. [5]
- c) (i) Describe regenerative braking. [4]  
(ii) Hence, highlight any three advantages of regenerative braking. [3]
- d) In power electronic systems with rectifier front-ends, describe with the aid of diagram, a means to avoid transient inrush currents at starting. [3]
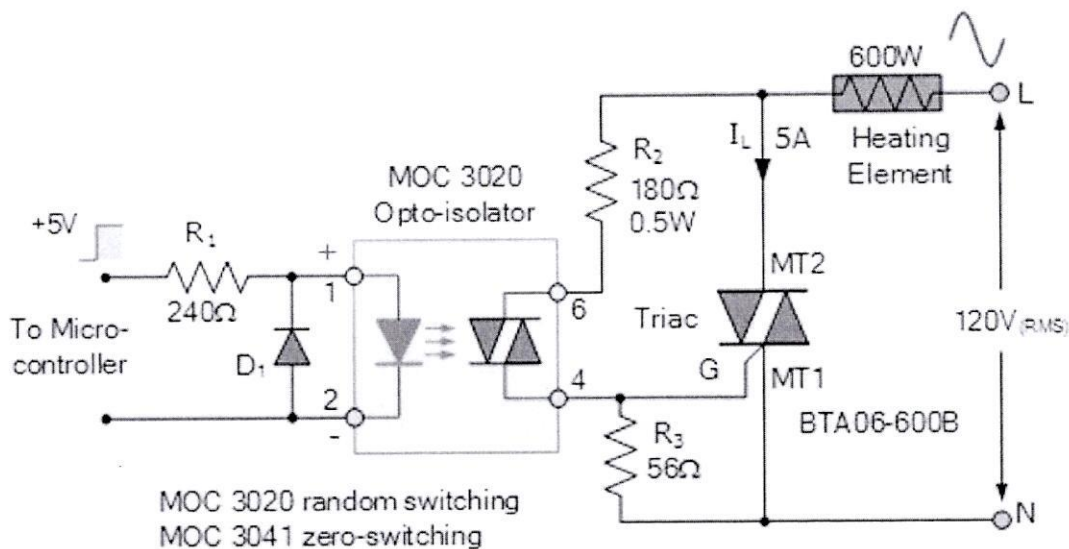
## Question 6


- With the aid of a block diagram, highlight the stages for an instrumentation measuring system. [4]
- With the aid of a circuit diagram and supporting equations, describe the operation of the stepdown converter. [7]
- Describe the operation of the AC Solid State Relay Circuit below. [5]



- A current  $i_s$ , of square waveform is shown in Figure below. Hint, [3]

From Fourier analysis,  $i_s(t)$  can be expressed as
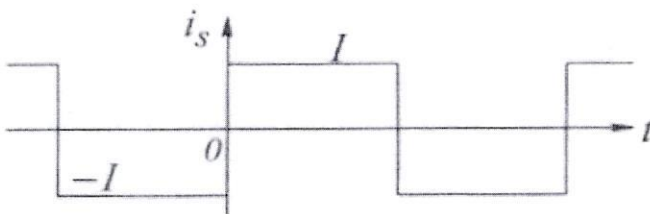
$$i_s = \frac{4}{\pi} I (\sin \omega_1 t + \frac{1}{3} \sin 3\omega_1 t + \frac{1}{5} \sin 5\omega_1 t + \frac{1}{7} \sin 7\omega_1 t + \dots)$$



- Calculate and plot its fundamental frequency component and its distortion component. [3]
- What is the %THD associated with this waveform? [1]

The fundamental frequency component and the distortion component are plotted in Figure below.

### Question 7

- a) Briefly describe the, Deleterious Effects of Harmonic Distortion and a Poor Power Factor. [6]
- b) With the aid of waveforms and circuit diagram, describe the principle of operation of the flyback converter. [10]
- c) Describe four characteristics required for the selection of a driving motor. [4]