

**BINDURA UNIVERSITY OF SCIENCE EDUCATION**

**FACULTY OF SCIENCE AND ENGINEERING**

**DEPARTMENT: ENGINEERING AND PHYSICS**

17 APR 2025

**PROGRAMME: BSc Honours Degree in Electronics Engineering**

**EEE2208: ELECTRONIC DRIVES AND POWER ELECTRONICS APPLICATIONS**

**DURATION: 3 hours**

**TOTAL MARKS: 100**

**INSTRUCTIONS TO CANDIDATES**

The paper contains 7 questions, answer any FIVE questions. Each carries 20 marks

Only calculator is permitted

---

**Question 1**

- a) Why is it important to maintain a high power factor in electrical systems? [4]
- b) Explain the working principle of a diode. [6]
- c) What are the advantages of Schottky diodes in power electronics applications? [10]

**Question 2**

- a) Describe the operation of a thyristor. [10]
- b) Explain industrial applications of thyristors. [10]

**Question 3**

- a) Compare the advantages and disadvantages of MOSFETs and IGBTs in power switching. [12]
- b) Explain why MOSFETs are preferred for high-frequency applications. [8]

**Question 5**

- a) Explain the types of Uninterruptible Power Supplies (UPS) systems. [14]
- b) Functional Block Diagram of switch-mode power (SMPS) supplies in UPS. [6]

**Question 6**

- a) Describe the working principle of static VAR compensators. [10]
- b) Explain their role in reactive power management. [6]

- c) Explain the effects of harmonics on power system components.

[4]

**Question 7**

- a) Describe the speed control of a shunt motor using rheostatic methods. [10]
- b) Calculate the speed if the back EMF is 220V, armature resistance is  $0.5\Omega$ , and armature current is 10A. [10]

**END OF EXAM**