

**BINDURA UNIVERSITY OF SCIENCE EDUCATION**  
**FACULTY OF SCIENCES AND ENGINEERING**  
**DEPARTMENT OF ENGINEERING AND PHYSICS**  
**ELECTRONIC ENGINEERING DEVICES AND CIRCUITS ANALYSIS**  
**EEE1203**

JUN 2025

Examination Paper

Time Allowed: 3 hours

Total Marks: 100

Special Requirements: Calculator, Graph Paper

Examiner's Name: S. Komichi

**INSTRUCTIONS**

1. Answer any FOUR questions only.
2. Each question carries 25 marks.
3. Show your steps clearly in any calculation.
4. Start the answers for each question on a fresh page.

**MARK ALLOCATION**

QUESTION	MARKS
1.	25
2.	25
3.	25
4.	25
5.	25
6.	25
7.	25
TOTAL	100

Page 1 of 8

### Question 1

Determine the dc resistance levels for the diode of Figure 1.1 below at

- (a)  $I_D = 2 \text{ mA}$
- (b)  $I_D = 20 \text{ mA}$
- (c)  $V_D = 10 \text{ V}$

[4], [4], [4]

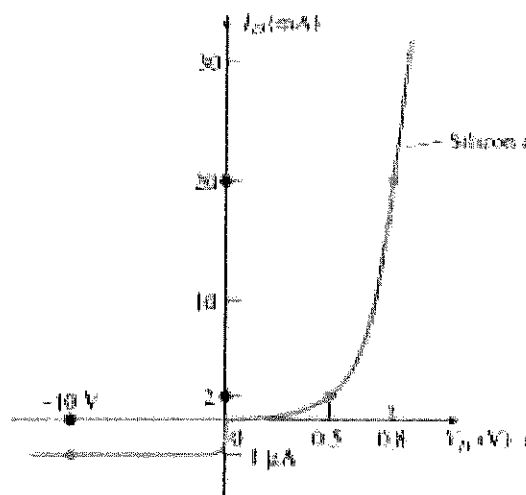


Figure 1.1 Diode Characteristics

- (d) (i) Design the voltage divider of Figure 1.2 below such that  $V_{R1} = 4V_{R2}$

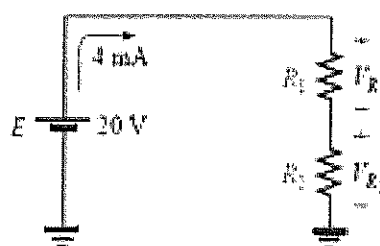


Figure 1.2: Voltage Divider

[5]

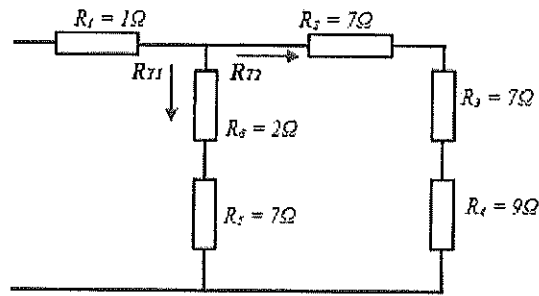


Figure 1.3: Resistor Network

(d) (ii) Calculate total resistances for circuit in Figure 1.3 above; also calculate branch resistances for the circuit. [2], [3], [3]

### Question 2

- a) For the series diode configuration of Figure 2.1 employing the diode characteristics of Figure 2.2 determine:
- $V_{DQ}$  and  $I_{DQ}$ .
  - $V_R$ . [3], [3], [4].

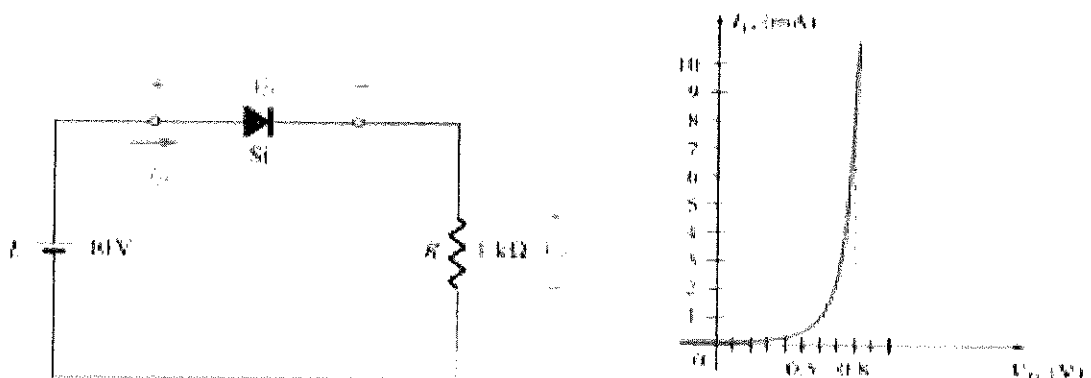


Figure 2.1: Series Diode and Characteristics

- b) Determine  $V_o$  and  $I_D$  for the series circuit of Figure 2.2 below.

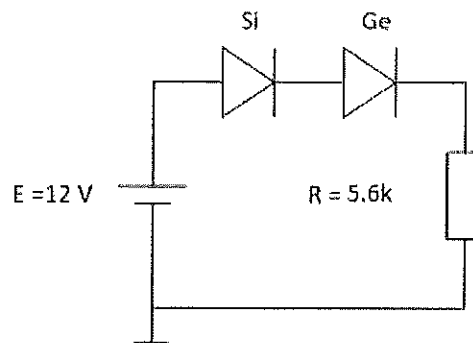


Figure 2.2: Diodes Network

[3], [3]

- c) For the circuit below Figure 1.4 determine  $V_2$ , Current  $I$ , resistors  $R_1$  and  $R_3$  using KVL.

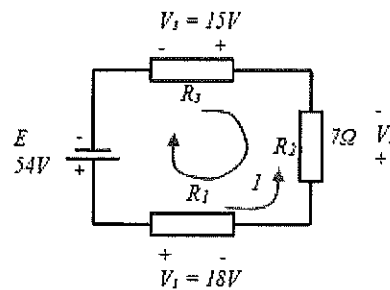


Figure 2.3: Resistor Network

[4], [4]

### Question 3

- The emf of a battery is 22.5V. How much charge flows if energy transferred is 90J? What is the current if the transfer time is 1.5 minutes? [6]
- Determine the resistance of a 30m copper wire with a diameter of 0.032cm and resistivity of  $1.723 \times 10^{-8}$ . [6]
- What is the pd across a lamp that dissipates 1000J in 10 seconds if current is 0.4A? [6]
- Draw the common collector transistor configuration circuit clearly showing the current directions. [7]

#### Question 4

a) Find the indicated currents and voltages for the network of Figure 4.1 below. Also find current in each branch ( $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_4$  and  $I_5$ ) that is current through each resistor as well as  $V_1$  and  $V_5$ . [3], [3], [3], [3], [3]

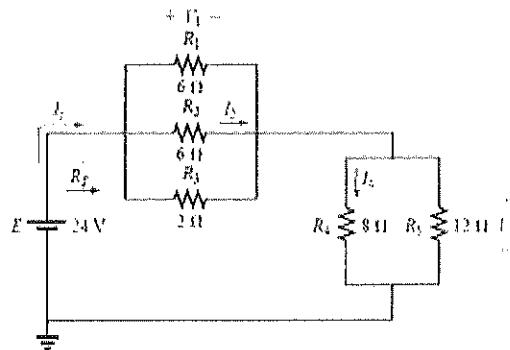


Figure 4.1: Resistor Networks

b) Determine the voltage  $V_o$  for the network of Figure 4.2 below. [5]

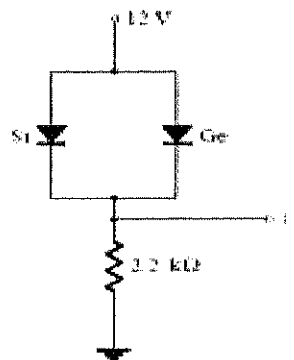


Figure 4.2: Diode Network

Calculate the total current through the  $4k\Omega$  resistor and the currents through the Si and the Ge diodes for the circuit in Figure 1.6. [2], [2], [1]

### Question 5

- a) Given the load line of Figure 5.1 and the defined Q-point, determine the required values of  $V_{CC}$ ,  $R_C$ , and  $R_B$  for a fixed-bias configuration. [4], [4], [5]

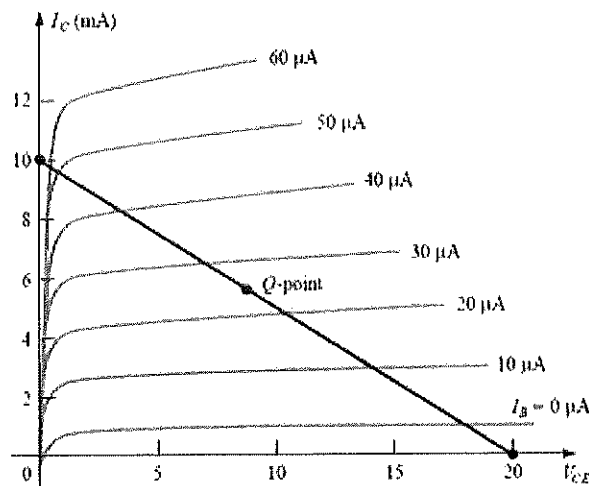


Figure 5.1: Load Line Analysis

- b) For the emitter bias network of Figure 5.2 below, determine:

- (i)  $I_B$ .
- (ii)  $I_C$ .
- (iii)  $V_{CE}$ .
- (iv)  $V_C$ .
- (v)  $V_E$ .
- (vi)  $V_B$ .

[2], [2], [2], [2], [2], [2]

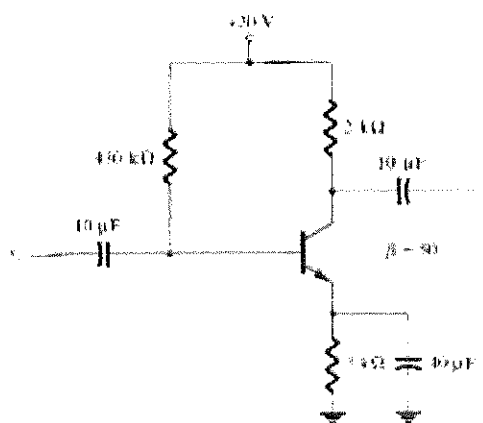


Figure 5.2: Emitter Stabilized Circuit

### Question 6

a)

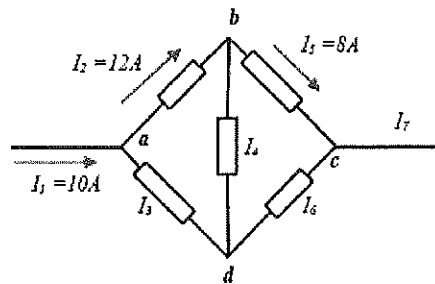


Figure 6.1: Resistor Network

- a) Find the magnitude and direction of the currents in Figure 6.1  $I_3$ ,  $I_4$ ,  $I_6$  and  $I_7$  above. [8]
- b) Give two differences between the Rectifier diodes and Zener diodes. [4]
- c) (i) For the network of Figure 6.2 below, determine the range of  $R_L$  and  $I_L$  that will result in  $V_{RL}$  being maintained at 10 V. [3], [3], [3], [4]  
 (ii) Determine the maximum and minimum wattage rating of the diode in Figure 6.2 below.

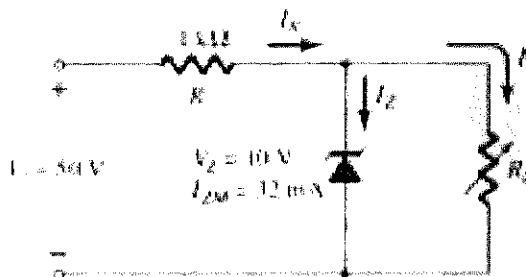


Figure 6.2: Zener Regulator

**Question 7**

- a) Determine the quiescent levels of  $I_{CQ}$  and  $V_{CEQ}$  for the network of Figure 7.1 below [13]

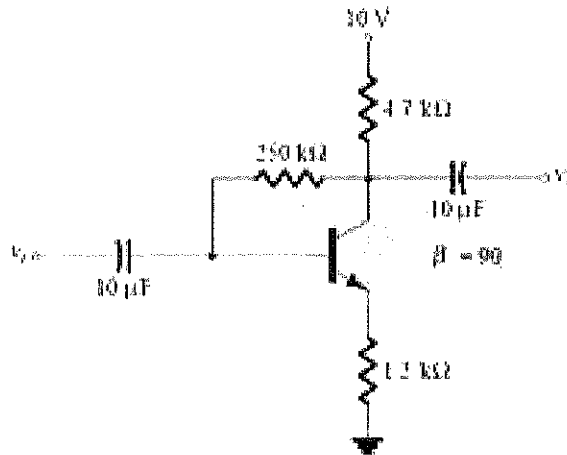


Figure 7.1: Bias Network

**Question 7**

- b) Determine the dc bias voltage  $V_{CE}$  and the current  $I_C$  for the voltage-divider configuration of Figure 7.2 below. [12]

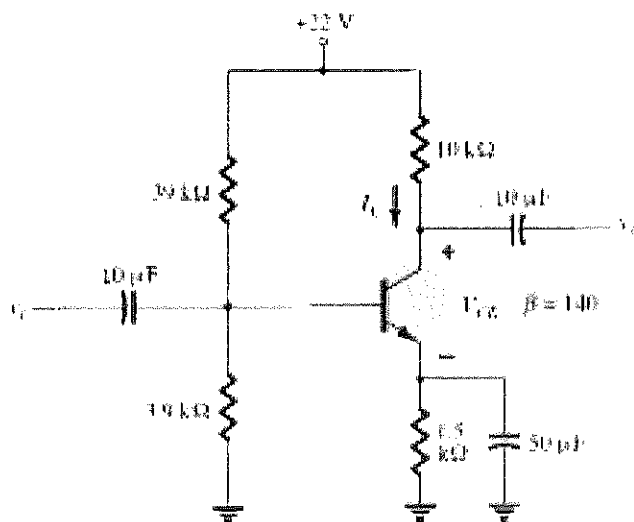


Figure 7.2: Voltage Divider Circuit