

BINDURA UNIVERSITY OF SCIENCE EDUCATION
FACULTY OF SCIENCE AND ENGINEERING
DEPARTMENT: ENGINEERING AND PHYSICS
PROGRAMME BSc HONOURS DEGREE IN NETWORK ENGINEERING
COURSE CODE PH203 (1): CIRCUIT ANALYSIS
DURATION: 3 HOURS TOTAL MARKS: 100

INSTRUCTIONS TO CANDIDATES

NOV 2024

Answer **question one** in Section A and **any three** questions from Section B. Section A carries 40 marks and each question in Section B carries 20 marks.

SECTION A

- 1 (a) Convert the following from rectangular to polar form: $C = 3 + j 4$. [4]
- (b) Determine the sum of $C_1 = 2 + j 4$ and $C_2 = 3 + j 1$. [4]
- (c) Find the product of C_1 and C_2 if $C_1 = 2 + j 3$ and $C_2 = 5 + j 10$. [4]
- (d) Given that $C_1 = 5 \angle 20^\circ$ and $C_2 = 10 \angle 30^\circ$, calculate the product of C_1 and C_2 . [4]
- (e) Transform the following sinusoid in time domain to phasor domain: $i = 6\cos(50t - 40^\circ)$ A. [5]
- (f) Convert the sinusoid corresponding to the following phasor to time domain: $V = -10 \angle 30^\circ$ V. [5]
- (g) The instantaneous current of an ac sinusoidal current is given by $= I_m \cos \omega t$. Show that $I_{rms} = \frac{I_m}{\sqrt{2}}$. [6]
- (h) Distinguish between ideal and practical sources in electric circuit theory. [2]
- (i) Use resistor colour codes to determine the resistances of resistors with the following band colours:
 - (1) green, brown, blue, silver. [2]
 - (2) yellow, violet, silver. [2]
 - (3) grey, red, gold. [2]

SECTION B

- 2 (a) Find the equivalent resistance between A and B in Fig. 2.1 using the Wye-Delta transformation. [18]

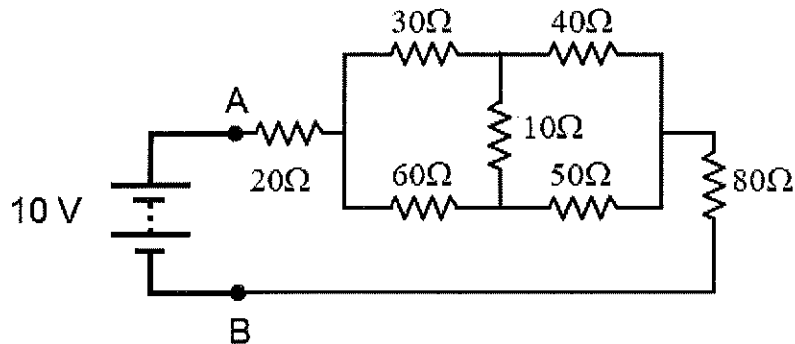


Fig. 2.1

- (b) Hence determine the value of the current supplied by the power source. [2]
- 3 (a) Determine the current through the $1\ \Omega$ resistor in the circuit in Fig. 3.1 using Superposition Theorem. [16]

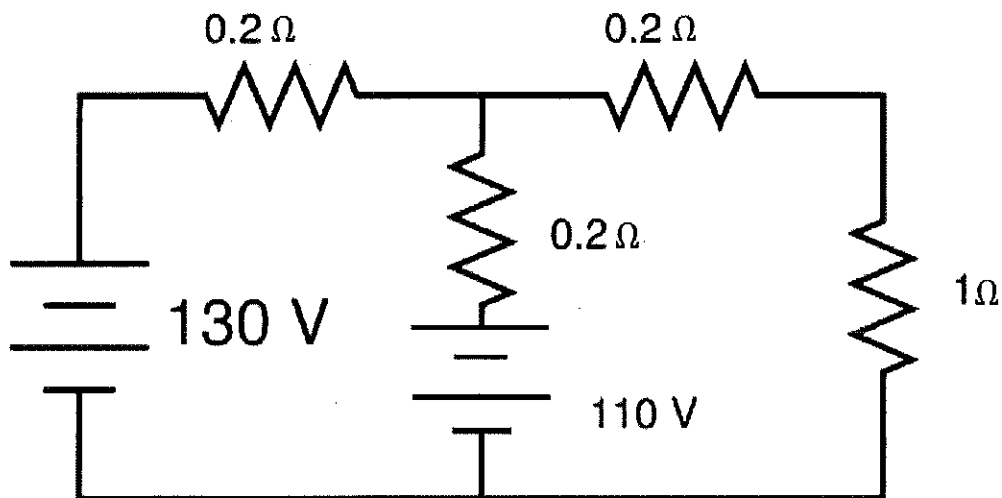


Fig. 3.1

- (b) Calculate the amount of heat energy dissipated in the $1\ \Omega$ resistor in part (a) over a time interval of 1 hour. [4]

4

In the network of Fig. 4.1, find the Thevenin voltage (V_{TH}), Thevenin resistance (R_{TH}) and the load current I_L flowing through and load voltage (V_L) across the load resistor $R_L = 5\text{ k}\Omega$ using Thevenin's Theorem. [20]

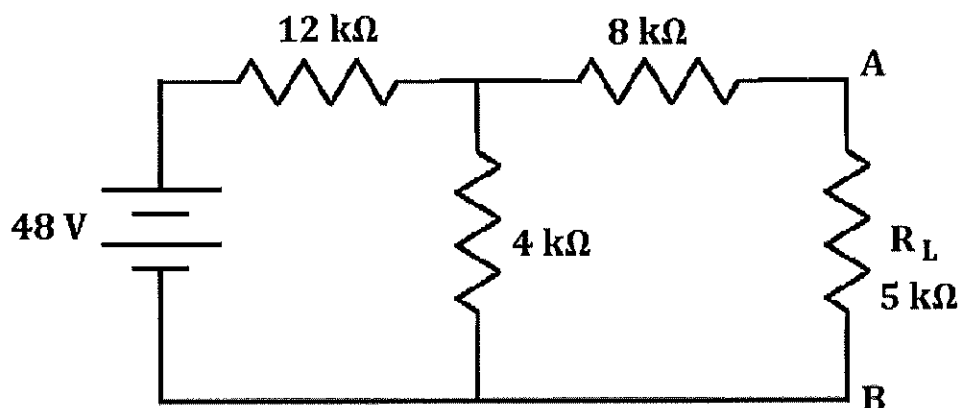


Fig. 4.1

5

In the network of Fig. 5.1, find the Norton current (I_N), Norton resistance (R_N) and the load current I_L flowing through and load voltage (V_L) across the load resistor $R_L = 1.5\text{ }\Omega$ using Norton's Theorem. [20]

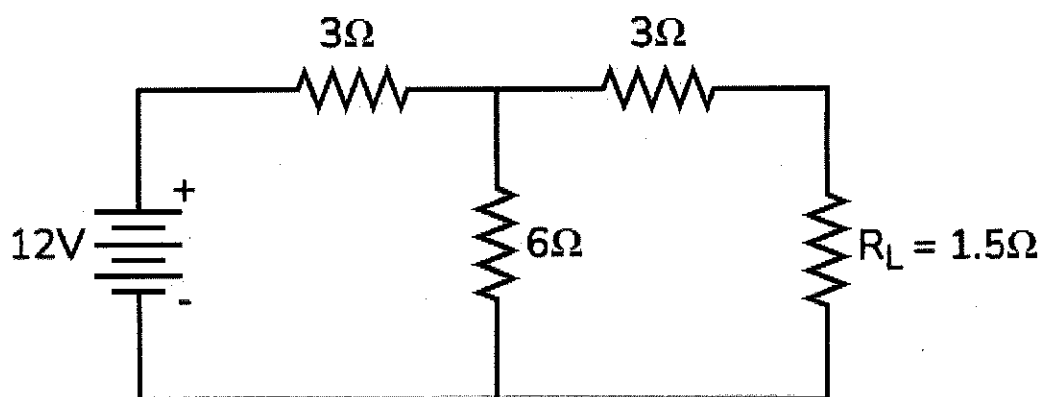


Fig. 5.1

6

A current waveform is described by the function: $i(t) = \begin{cases} 5t, & 0 < t < 2 \\ -10, & 2 < t < 4 \end{cases}$ as shown in Fig. 6.1.

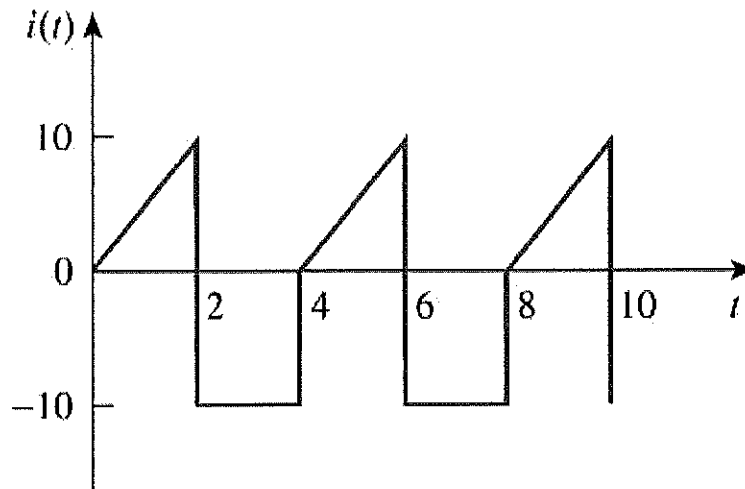


Fig. 6.1

The current is passed through a $2\text{-}\Omega$ resistor.

- (a) Find the rms value of the current. [18]
- (b) Calculate the average power absorbed by the resistor. [2]